

O módulo Serial LCD Controller (SLCDC) implementa a interface com o LCD, fazendo a receção em série da informação enviada pelo módulo de controlo e entregando-a posteriormente ao LCD

1 Modulo SLCDC

O módulo SLCDC recebe em série uma mensagem constituída por nove (9) bits de informação e um (1) bit de paridade. A comunicação com este módulo realiza-se segundo o protocolo ilustrado na Figura 1, em que o bit RS é o primeiro bit de informação e indica se a mensagem é de controlo ou dados. Os seguintes oito (8) bits contêm os dados a entregar ao LCD. O último bit contém a informação de paridade par, utilizada para detetar erros de transmissão.

 


Figura 1 – Diagrama de blocos do módulo SLCDC

 


Figura 2 – Protocolo de comunicação com o módulo Serial LCD Controller

2 Interface com o Control

Implementou-se os módulos TUI e LCD em *software*, recorrendo a linguagem Kotlin, o bloco Serial Receiver e o bloco LCD Dispatcher em *hardware*, recorrendo a linguagem VHDL.

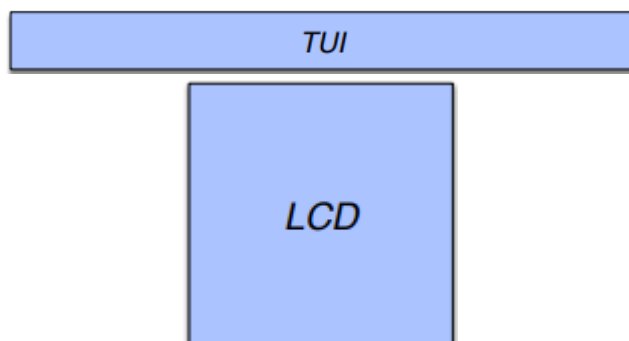


Figura 3 Classe LCD e TUI

As classes LCD e TUI desenvolvidas são descritas nas secções 2.1. e 2.2, e o código fonte desenvolvido nos Anexos C e B, respetivamente.

2.1 Classe LCD

- Init, que inicia a classe
- writeByteSerial, escreve um byte (comando ou dados) no LCD em série
- writeByte, chama a função writeByteParallel e escreve um byte de comando/dados no LCD
- writeCMD, chama a função writeByte e escreve um comando no LCD
- writeDATA, chama a função writeByte e escreve um dado no LCD
- write, recebe um char e chama a função writeDATA e escreve um carácter na posição corrente
- write, recebe uma string e chama a função write e escreve uma string na posição corrente
- cursor, recebe uma linha e uma coluna e envia um comando para posicionar o cursor nessa posição
- clear, envia um comando para limpar o ecrã e posicionar o cursor em (0,0)
- Invader, spaceShip e loadCustomChars, são responsáveis pelo desenho da nave e do invader e, pela customização dos mesmos

2.2 Classe TUI

- Escrever, é responsável pela escrita no LCD na parte direita do ecrã e ir decrementando as colunas.
- Align, é responsável por escrever o texto que é passado na linha e na coluna como parâmetro, usando funções do LCD
- AlignLeft, é responsável por escrever o texto à esquerda do LCD que é passado na linha como parâmetro, usando funções do LCD

- AlignRight, é responsável por escrever o texto à direita do LCD que é passado na linha como parâmetro, usando funções do LCD
- AlignMiddle, é responsável por escrever o texto alinhado ao centro do LCD que é passado na linha como parâmetro, usando funções do LCD
- forWaitKey, é responsável por chamar a função do KBD que espera por uma tecla passado como timeout
- clrLCD, é responsável por limpar o LCD
- cursor, é responsável por colocar o cursor na linha e coluna que são passadas como parâmetro usando função do LCD
- .init, inicia o KBD e o LCD

3 Serial Receiver

O bloco Serial Receiver do módulo SLDC é constituído por quatro blocos principais: i) um bloco de controlo; ii) um bloco conversor série paralelo; iii) um contador de bits recebidos; e iv) um bloco de validação de paridade, designados por Serial Control, Shift Register, Counter e Parity Check respetivamente.

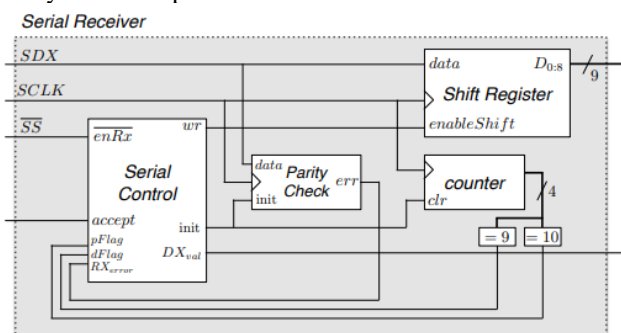


Figura 4 – Diagrama de blocos do bloco Serial Receiver

- O Serial Control é uma máquina de estados com 5 estados, Initializing, Starting, Waiting, Accepted e ItsDone. Começa por ativar o init no primeiro estado, dando assim init ao Parity Check (reset) e clear ao Counter, quando o sinal enRX tiver a '0', a máquina transita para o próximo estado Starting ativando o sinal wr, dando assim enableShift ao Shift Register.

Para transitar para o próximo estado Waiting, é feita novamente a verificação do sinal enRX, se este tiver o valor '1' retornará para o estado inicial Initializing, se o sinal enRX tiver a '0', e o sinal dFlag tiver a '1' será feita a transição.

Após isto, é feita novamente a verificação do sinal enRX, caso este esteja ativo, retornará para o estado inicial, Initializing se o sinal estiver a '0', é feita a verificação do sinal pFlag, se este tiver a '1', a máquina transita para o estado Accepted.

Neste estado, é feita uma verificação do sinal RXerror onde, caso este esteja ativo, retornará para o estado inicial Initializing, se o sinal estiver a '0', passará para o próximo e último estado ItsDone.

Neste último estado o sinal DXval é ativo e, é feita uma verificação do sinal Accept, caso este esteja a '1' retornará ao estado inicial.

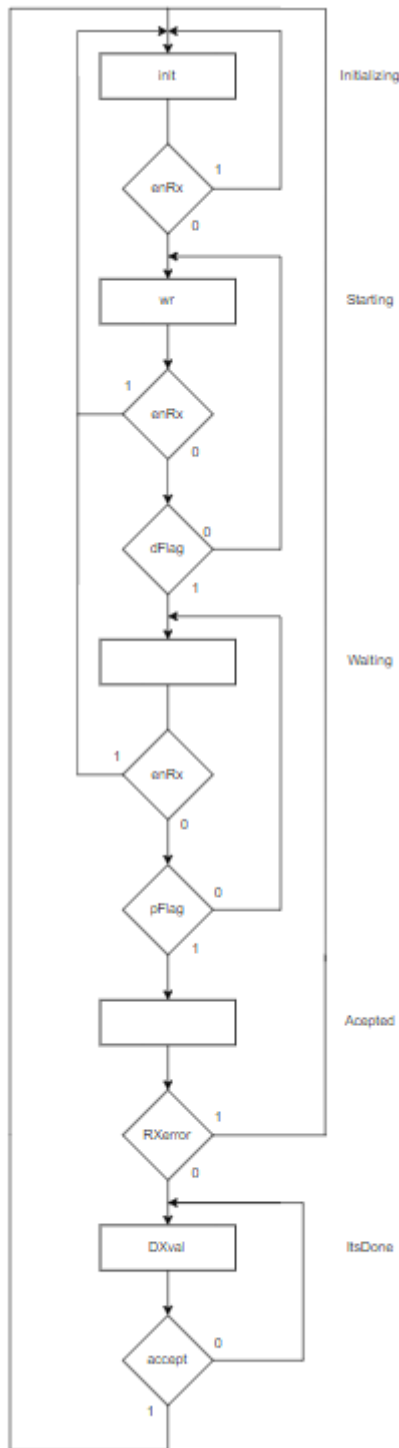


Figura 5 – Máquina de estados do Serial Control

LCD, através da ativação do sinal WrL . Este bloco é apenas constituído pelo Control.

- O LCDDispatcherControl é uma máquina de estados com três estados, WaitingDval, ReceivingDval e DoneReceived. No primeiro estado WaitingDval, começa por verificar se o sinal Dval encontra-se a '1', se sim, significa que a trama foi recebida e a máquina transita para o próximo estado sendo este o ReceivingDval. Neste estado, o sinal Wrl é ativo e transita para o estado DoneReceived onde o sinal Wrl deixa de estar ativo, deixando ativo o sinal done ativo, neste estado, o Dval é novamente verificado, porém neste caso se este tiver a '0' retornará para o estado inicial WaitingDval, significando que a trama já foi processada e a máquina poderá esperar por uma nova trama.

4 LCD Dispatcher

O bloco LCD Dispatcher é responsável pela entrega das tramas válidas recebidas pelo bloco Serial Receiver ao

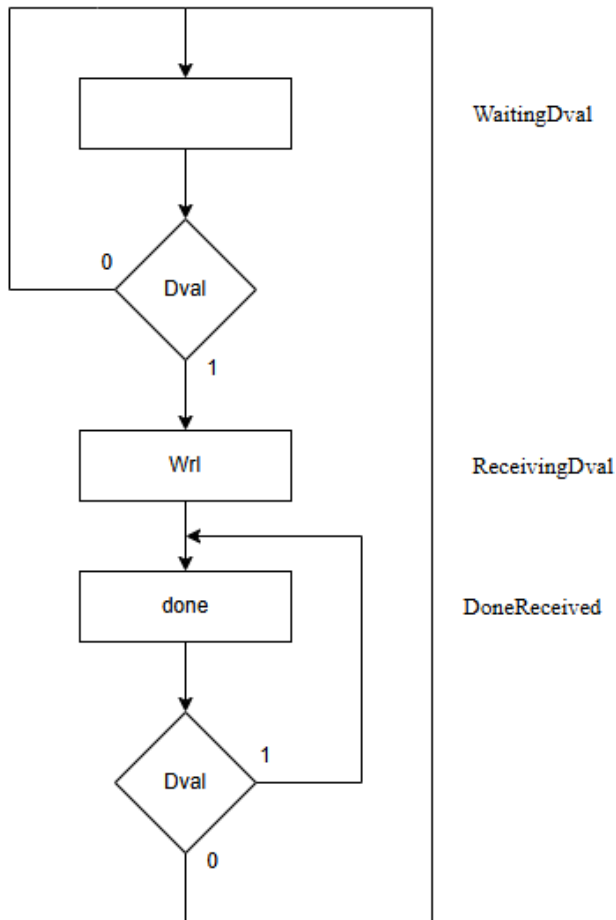


Figura 6 – Máquina de estados do LCD Dispatcher Control

5 Conclusão

Com a implementação deste módulo foi possível a interação com o LCD a partir de dois blocos: Serial Receiver e LCD Dispatcher. Estes dois blocos têm a função de ler e transmitir a mensagem enviada pelo bloco de controlo até ao LCD.

A. Descrição VHDL do bloco SLCDC

Código VHDL do SLCDC:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity SLCDC is
    port(
        SS : in std_logic;
        Reset : in std_logic;
        SCLK : in std_logic;
        Clk : in std_logic;
        SDX : in std_logic;
        WrL : out std_logic;
        DoutSLCDC: out std_logic_vector(8 downto 0)
    );
end SLCDC;

architecture structural of SLCDC is
    component SerialReceiver is

```

```
port(
    Reset : in std_logic;
    SDX : in std_logic;
    Clk : in std_logic;
    SCLK : in std_logic;
    SS : in std_logic;
    accept : in std_logic;
    D : out std_logic_vector(8 downto 0);
    DXval : out std_logic
);
end component;
component LCDDispatcher is
    port(
        Dval : in std_logic;
        Din : in std_logic_vector(8 downto 0);
        WrL : out std_logic;
        Dout : out std_logic_vector(8 downto 0);
        clk : in std_logic;
        reset : in std_logic;
        done : out std_logic
    );
end component;
signal done_exit : std_logic;
signal D_exit : std_logic_vector(8 downto 0);
signal DXval_exit : std_logic;

begin

    LCD: LCDDispatcher port map (Dval => DXval_exit, Din => D_exit, Wrl => WrL, Dout => DoutSLCDC, done =>
done_exit,clk => Clk, reset => Reset );

    SR : SerialReceiver port map (Reset => Reset, SDX => SDX, Clk => Clk, SCLK => SCLK, SS => SS, accept => done_exit,
D => D_exit, DXval => DXval_exit);

end structural;
```

Código VHDL do SerialReceiver:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
entity SerialReceiver is
```

```
    port(
```

```
        Reset : in std_logic;
```

```
        SDX : in std_logic;
```

```
        Clk : in std_logic;
```

```
        SCLK : in std_logic;
```

```
        SS : in std_logic;
```

```
        accept : in std_logic;
```

```
        D : out std_logic_vector(8 downto 0);
```

```
        DXval : out std_logic
```

```
    );
```

```
end SerialReceiver;
```

```
architecture structural of SerialReceiver is
```

```
    component ShiftRegisterSerialReceiver is
```

```
        port(
```

```
            reset : in std_logic;
```

```
            data: in std_logic;
```

```
            SCLK: in std_logic;
```

```
            E: in std_logic;
```

```
            D: out std_logic_vector(8 downto 0)
```

```
        );
```

```
    end component;
```

```
    component Counter is
```

```
        port(
```

```
            PL:in std_logic;
```

```
            CE:in std_logic;
```

```
            CLK:in std_logic;
```

```
            Data_in: in std_logic_vector(3 downto 0);
```

```
            RESET: in std_logic;
```

```
            TC: out std_logic;
```

```
            Q:out std_logic_vector(3 downto 0)
```

```
        );
```

```
    end component;
```

```
    component ParityCheck is
```

```
        port(
```

```
            data : in std_logic;
```

```
Sclk : in std_logic;
init : in std_logic;
err : out std_logic

);
end component;
component SerialControl is
    port(
        enRx : in std_logic;
        accept : in std_logic;
        pFlag : in std_logic;
        dFlag : in std_logic;
        RXerror : in std_logic;
        wr : out std_logic;
        init : out std_logic;
        Reset : in std_logic;
        Clk : in std_logic;
        DXval : out std_logic
    );
end component;
component Equal9 IS
    port(
        Q: in STD_LOGIC_VECTOR(3 downto 0);
        TC: out STD_LOGIC
    );
end component;
component Equal10 IS
    port(
        Q: in STD_LOGIC_VECTOR(3 downto 0);
        TC: out STD_LOGIC
    );
end component;

signal ParitCheck_err_exit : std_logic;
signal SerialControl_init_exit : std_logic;
signal SerialControl_wr_exit : std_logic;
signal CounterSerialReceiver_exit : std_logic_vector(3 downto 0);
signal dflag_9: std_logic;
signal pflag_10: std_logic;
```

begin

Shift: ShiftRegisterSerialReceiver port map (data=>SDX ,SCLK=>SCLK ,E => SerialControl_wr_exit,D=>D, reset => Reset);

Count: Counter port map (PL => '0', CE => '1', CLK => SCLK, Data_in => "0000", RESET => SerialControl_init_exit, Q => CounterSerialReceiver_exit);

Parity: ParityCheck port map (data => SDX, Sclk => SCLK, init => SerialControl_init_exit, err => ParitCheck_err_exit);

Controle: SerialControl port map (enRX => SS, accept => accept, pFlag => pflag_10 , dFlag => dflag_9, RXerror => ParitCheck_err_exit, wr => SerialControl_wr_exit, init => SerialControl_init_exit, DXval => DXval, Clk => Clk, Reset => Reset);

EQ1: Equal9 port map(Q => CounterSerialReceiver_exit,TC => dflag_9);

EQ2: Equal10 port map(Q => CounterSerialReceiver_exit,TC => pflag_10);

end structural;

Código VHDL do ShiftRegisterSerialReceiver:

LIBRARY ieee;

USE ieee.std_logic_1164.all;

entity ShiftRegisterSerialReceiver is

port(

reset : in std_logic;

data: in std_logic;

SCLK: in std_logic;

E: in std_logic;

D: out std_logic_vector(8 downto 0)

);

end ShiftRegisterSerialReceiver;

architecture structural of ShiftRegisterSerialReceiver is

component FFD IS

PORT(

CLK : in std_logic;

RESET : in STD_LOGIC;

SET : in std_logic;


```
D : IN STD_LOGIC;  
EN : IN STD_LOGIC;  
Q : out std_logic  
);  
end component;
```

```
signal saidaFFD1: std_logic;  
signal saidaFFD2: std_logic;  
signal saidaFFD3: std_logic;  
signal saidaFFD4: std_logic;  
signal saidaFFD5: std_logic;  
signal saidaFFD6: std_logic;  
signal saidaFFD7: std_logic;  
signal saidaFFD8: std_logic;  
signal saidaFFD9: std_logic;
```

```
begin
```

```
FFD1: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>data ,EN=>E ,Q=>saidaFFD1);  
FFD2: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD1,EN=>E,Q=>saidaFFD2);  
FFD3: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD2,EN=>E,Q=>saidaFFD3);  
FFD4: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD3,EN=>E,Q=>saidaFFD4);  
FFD5: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD4,EN=>E,Q=>saidaFFD5);  
FFD6: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD5,EN=>E,Q=>saidaFFD6);  
FFD7: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD6,EN=>E,Q=>saidaFFD7);  
FFD8: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD7,EN=>E,Q=>saidaFFD8);  
FFD9: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD8,EN=>E,Q=>saidaFFD9);
```

```
D(8)<= saidaFFD1;  
D(7)<= saidaFFD2;  
D(6)<= saidaFFD3;  
D(5)<= saidaFFD4;  
D(4)<= saidaFFD5;  
D(3)<= saidaFFD6;  
D(2)<= saidaFFD7;  
D(1)<= saidaFFD8;  
D(0)<= saidaFFD9;
```

end structural;

Código VHDL do ParityCheck:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity ParityCheck is
    port(
        data : in std_logic;
        Sclk : in std_logic;
        init : in std_logic;
        err : out std_logic
    );
end ParityCheck;

architecture structural of ParityCheck is

    component Counter is
        port(
            PL:in std_logic;
            CE:in std_logic;
            CLK:in std_logic;
            Data_in: in std_logic_vector(3 downto 0);
            RESET: in std_logic;
            TC: out std_logic;
            Q:out std_logic_vector(3 downto 0)
        );
    end component;

    signal SaidaB : std_logic_vector(3 downto 0);

begin

    CounterUp : Counter port map (PL => '0', CE => data, CLK => Sclk, Data_in => "0000", Q => SaidaB, RESET => init);
    err <= SaidaB(0);

end structural;
```

Código VHDL do SerialControl:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity SerialControl is
    port(
        enRx : in std_logic;
        RESET : in std_logic;
        accept : in std_logic;
        pFlag : in std_logic;
        dFlag : in std_logic;
        RXerror : in std_logic;
        clk : in std_logic;
        wr : out std_logic;
        init: out std_logic;
        DXval : out std_logic
    );
end SerialControl;

architecture behavioral of SerialControl is

    type STATE_TYPE is (Intializing, Starting, Waiting, Accepted, ItsDone);

    signal currentState, NextState: STATE_TYPE;

begin

    currentState <= Intializing when RESET = '1' else NextState when rising_edge(clk);

    GenerateNextState:
    process (currentState, enRx, accept, pFlag, RXerror, dFlag)
    begin
        case currentState is
            when Intializing => if (enRx = '0') then
                NextState <=
                Starting;
            else

```

```

NextState <=

Intializing;

end if;

when Starting => if (enRx = '1') then

NextState <=

Intializing;

elsif (dFlag = '1') then

NextState <=

Waiting ;

else

NextState <=

Starting;

end if;

when Waiting => if (enRx = '1') then

NextState <=

Intializing;

elsif(pFlag = '1') then

NextState <=

Accepted;

else

NextState <=

Waiting;

end if;

when Accepted => if(RXerror = '0') then

NextState <=

ItsDone;

else

NextState <=

Intializing;

end if;

when ItsDone => if(accept = '1') then

NextState <=

Intializing;

else

```

```

NextState <=

ItsDone;

end if;

end case;

end process;

wr <= '1' when(currentState = Starting) else '0';
init <= '1' when(currentState = Intializing) else '0';
DXval <= '1' when (currentState = ItsDone) else '0';

end behavioral;
```

Código VHDL do LCDDispatcher:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity LCDDispatcher is
    port(
        Dval : in std_logic;
        reset : in std_logic;
        clk : in std_logic;
        Din : in std_logic_vector(8 downto 0);
        WrL : out std_logic;
        Dout : out std_logic_vector(8 downto 0);
        done : out std_logic
    );
end LCDDispatcher;

architecture structural of LCDDispatcher is
    component LCDDispatcherControl is
        port(
            clk : in std_logic;
            reset : in std_logic;
            Dval : in std_logic;
            Wrl : out std_logic;
            done : out std_logic
        );
    end component;
begin
```

LCD: LCDDispatcherControl port map (Dval => Dval, clk => clk , Wrl => Wrl, done => done , reset => reset);

Dout <= Din;

end structural;

Código VHDL do LCDDispatcherControl:

LIBRARY ieee;

USE ieee.std_logic_1164.all;

entity LCDDispatcherControl is

port(

clk : in std_logic;

reset : in std_logic;

Dval : in std_logic;

Wrl : out std_logic;

done : out std_logic

);

end LCDDispatcherControl;

architecture behavior of LCDDispatcherControl is

type STATE_TYPE is (WaitingDval, ReceivingDval, DoneReceived);

signal currentState, nextState: STATE_TYPE;

begin

currentState <= WaitingDval when reset = '1' else nextState when rising_edge(clk);

GenerateNextState:

process(currentState, Dval)

begin

case currentState is

when WaitingDval => if (Dval = '1') then

nextState <=

ReceivingDval;

else

nextState <=

WaitingDval;

end if;

```

when ReceivingDval => NextState <= DoneReceived;

when DoneReceived =>
    if (Dval = '1') then
        NextState <= DoneReceived;
    else
        NextState <= WaitingDval;
    end if;
end case;
end process;

Wr1 <= '1' when (CurrentState = ReceivingDval)
else '0';

done <= '1' when (CurrentState = DoneReceived)
else '0';

end behavior;

```

B. Código Kotlin – TUI

```

import isel.leic.utils.Time

object TUI {

    var collumL0 = 16
    var collumL1 = 16

    fun escrever(str: String, left: Boolean, lines: Int, coll: Int) {
        if (left) {
            LCD.cursor(lines, coll)
            LCD.write(str)
            if (lines == 0) {
                collumL0 += 1
            } else {
                collumL1 += 1
            }
        } else {
            LCD.cursor(lines, coll)
            LCD.write(str)
        }
    }
}

```

```
        if (lines == 0) {
            collumL0 -= 1
        } else {
            collumL1 -= 1
        }
    }
}

fun align(line : Int, col : Int, c : Char) {
    align(line, col, c.toString())
}

fun align(line : Int, col : Int, txt : String) {
    LCD.cursor(line, col)
    LCD.write(txt)
}

fun alignLeft(line : Int, c : Char) {
    alignLeft(line, c.toString())
}

fun alignLeft(line : Int, txt : String) {
    if(txt.length <= 15) {
        LCD.cursor(line, 0)
        LCD.write(txt)
    }
}

fun alignRigth(line : Int, str : String) {
    if(str.length < LCD.COLS) {
        LCD.cursor(line, LCD.COLS - str.length)
        LCD.write(str)
    }
}

fun alignMiddle(line : Int, c : Char) {
    alignMiddle(line, c.toString())
}

fun alignMiddle(line : Int, txt : String) {
    val halfTxt = LCD.COLS - txt.length
    if (halfTxt >= 0) {
        LCD.cursor(line, halfTxt / 2)
        LCD.write(txt)
    }
}

fun forWaitKey(timeout: Long) : Char {
    return KBD.waitKey(timeout)
}

fun clrLCD() {
    LCD.clear()
}

fun cursor(line: Int, col: Int) {
    LCD.cursor(line, col)
}

fun init() {
    KBD.init()
}
```



```
LCD.init()  
}  
}
```

B Código Kotlin – LCD

```
object LCD { // Escreve no LCD usando a interface a 4 bits.  
    //      const val LINES = 2  
    val COLS = 16 // Dimensão do display.  
    const val E_MASK = 0X20  
    const val RS_MASK = 0x10  
    const val CLK_MASK = 0X40  
    const val DATA_MASK = 0X0F  
    // Envia a sequência de iniciação para comunicação a 4 bits.  
    fun init() {  
        SerialEmitter.init()  
        writeCMD(0b00110000)  
        Time.sleep(15)  
        writeCMD(0b00110000)  
        Time.sleep(1)  
        writeCMD(0b00110000)  
        writeCMD(0b00111000)  
        writeCMD(0b00001000)  
        writeCMD(0b00000001)  
        writeCMD(0b00000110)  
        writeCMD(0b00001111)  
        loadCustomChars()  
    }  
    fun writeByteSerial(rs: Boolean, data: Int) {  
        val rS = if (rs) 1 else 0  
        SerialEmitter.send(addr = SerialEmitter.Destination.LCD, data.shl(1) + rS, 9)  
    }  
    // Escreve um byte de comando/dados no LCD  
    fun writeByte(rs: Boolean, data: Int) {  
        writeByteSerial(rs, data)  
        //writeByteParallel(rs, data)  
    }  
  
    // Escreve um comando no LCD  
    fun writeCMD(data: Int) {  
        writeByte(false, data)  
    }  
    // Escreve um dado no LCD  
    fun writeDATA(data: Int) {  
        writeByte(true, data)  
    }  
    // Escreve um carácter na posição corrente.  
    fun write(c: Char) {  
        writeDATA(c.code)  
    }  
    // Escreve uma string na posição corrente.  
    fun write(text: String) {  
        for (c in text) {  
            write(c)  
        }  
    }  
    // Envia comando para posicionar cursor ('line':0..LINES-1 , 'column':0..COLS-1)
```

```
fun cursor(line: Int, column: Int) {  
    writeCMD((line * 0X40 + column) or 0x80)  
}  
// Envia comando para limpar o ecrã e posicionar o cursor em (0,0)  
fun clear() {  
    writeCMD(0b00000001)  
    cursor(0, 0)  
}  
fun invader() {  
    writeCMD (0x40)  
    writeDATA (0x1F)  
    writeDATA (0x1F)  
    writeDATA (0x15)  
    writeDATA (0x1F)  
    writeDATA (0x1F)  
    writeDATA (0x11)  
    writeDATA (0x11)  
    writeDATA (0x00)  
}  
fun spaceShip() {  
    writeCMD (0x48)  
    writeDATA (0x1E)  
    writeDATA (0x18)  
    writeDATA (0x1C)  
    writeDATA (0x1F)  
    writeDATA (0x1C)  
    writeDATA (0x18)  
    writeDATA (0x1E)  
    writeDATA (0x00)  
}  
fun loadCustomChars() {  
    invader()  
    spaceShip()  
}  
}
```