

O módulo *Keyboard Reader* é constituído por três blocos principais: *i*) o descodificador de teclado (*Key Decode*); *ii*) o bloco de armazenamento (designado por *Ring Buffer*); e *iii*) o bloco de entrega ao consumidor (designado por *Output Buffer*), de acordo com o diagrama representado na Figura 1. Neste caso, o módulo *Control*, implementado em software, é a entidade consumidora. Para esta primeira fase, o *Keyboard Reader* tem apenas o bloco de descodificação implementado (*Key Decode*) Figura 2a, fazendo diretamente a ligação com a entidade consumidora através do *UsbPort*.

 


Figura 1: Diagrama de blocos do módulo *Keyboard Reader*


1 Keyboard Reader

1.1 Key Decode


O bloco *Key Decode* implementa um descodificador de um teclado matricial 4x4 por *hardware*, sendo constituído por três sub-blocos: *i*) um teclado matricial de 4x4; *ii*) o bloco *Key Scanner*, responsável pelo varrimento do teclado; e *iii*) o bloco *Key Control*, que realiza o controlo do varrimento e o controlo de fluxo, conforme o diagrama de blocos representado na Figura 2a.

O controlo de fluxo de saída do bloco *Key Decode*, (para o módulo *Control*), define que o sinal K_{val} é ativado quando é detetada a pressão de uma tecla, sendo também disponibilizado o código dessa tecla no barramento $K_{0:3}$. Apenas é iniciado um novo ciclo de varrimento ao teclado quando o sinal K_{ack} for ativado e a tecla premida for libertada. O diagrama temporal do controlo de fluxo está representado na Figura 2b.

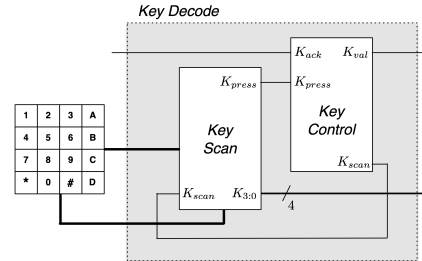O bloco *Key Scanner* foi implementado de acordo com o diagrama de blocos representado na Figura 3. Para este bloco, foi escolhida a 3ª versão, devido ao menor número de clocks (4) necessários para fazer o varrimento das 16 teclas presentes no teclado.




 (a) Diagrama de blocos do módulo *Key Decode*



(b) Diagrama temporal

Figura 2: Bloco *Key Decode*

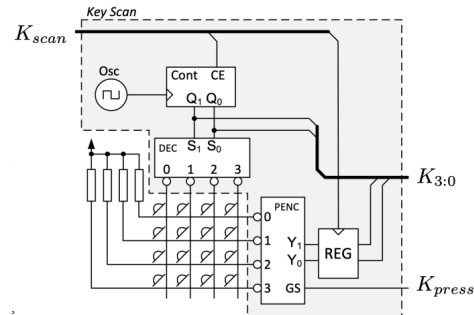

versão III

Figura 3: Diagrama de blocos do módulo *Key Scanner*

O bloco *Key Control* foi implementado pela máquina de estados representada em *ASM-chart* na Figura 4, de acordo com o funcionamento esperado do *KeyDecode*, acima mencionado.

A descrição *hardware* dos blocos *Key Reader*, *Key Decode*, *Key Scanner* e *Key Control* em *VHDL* encontra-se nos anexos *VHDL*.

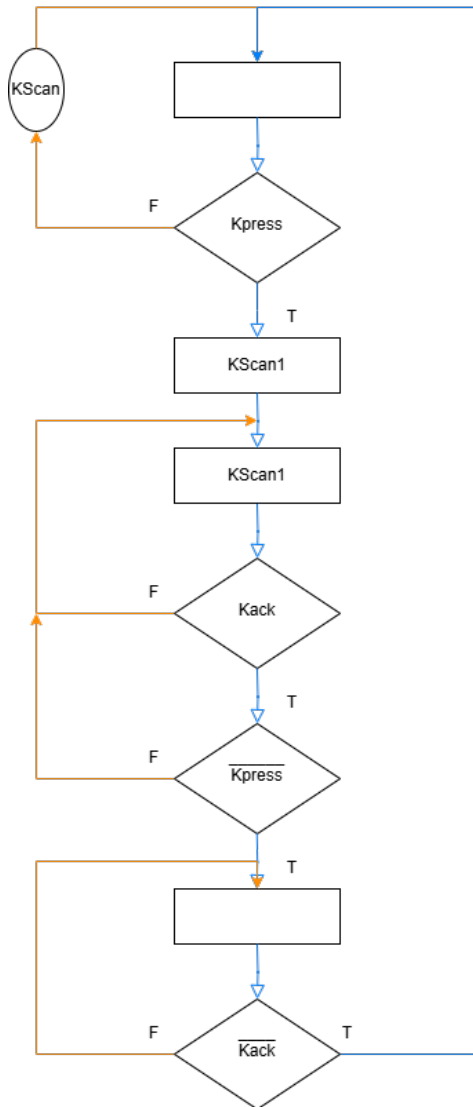


Figura 4: Máquina de estados do Key Control.
As linhas a laranja e azul representam o valor *false* e *true* respetivamente.

2 Control

Os módulos de Controlo são responsáveis pela lógica de alto nível, gerindo o estado do sistema, processando os dados e enviando informações para apresentar no LCD. Este tem como entradas um sinal de *input* válido do teclado, assim como a tecla correspondente a esse *input*, tendo por sua vez o dever de atualizar o estado do jogo (*ack*) de forma apro-

priada e comunicar com outros módulos a informação devida. Atua essencialmente como o “cérebro” do sistema, implementando o comportamento específico do jogo.

2.1 UsbPort

O *UsbPort* é a nossa forma de comunicação entre o teclado matricial e o módulo de *Control*. Esta ligação teve as entradas e saídas definidas de acordo com o ficheiro de texto *hardware.simul* Figura5 presente no projeto em *kotlin*.

```

#Generic modules to activate from Simulator
UsbPort = UsbPort
kbd = Keyboard("1234567890*",4,4,0)
lcd = LCD

#-----
#Keyboard Reader
#-----
1 -> kbd.os
kbd.k[0:3] -> UsbPort.I[1-4]
kbd.val -> UsbPort.ID
UsbPort.O0 -> kbd.ack

#-----
#LCD
#-----
#Serial Receiver
UsbPort.O[1-4] -> lcd.O[4-7]
UsbPort.O0 -> lcd.ps
UsbPort.O7 -> lcd.s
  
```

Figura 5: Configurações para a Simulação

2.2 HAL

O *HAL* é uma camada de abstração que permite separar as camadas superiores do software dos detalhes específicos do hardware usado. É no *HAL* que temos as ferramentas para usar os *bits* que entram e saem do *UsbPort*, ferramentas estas como *writeBits()*, *readBits()* fazer ref para o código do *HAL*. Ao encapsular estas funcionalidades, a *HAL* permite que os restantes módulos (como o *Scanner* do teclado ou o *Control* do jogo) interajam com o hardware de forma simplificada, sem depender dos detalhes técnicos do hardware específico utilizado. Esta abordagem promove a portabilidade do código e facilita a manutenção e evolução do sistema.

2.3 KBD

O *KBD* é a correspondência em *software* ao teclado matricial que queremos implementar. É aqui que decidimos os caracteres que queremos reproduzir no *display* e como é que chegamos ao código representado por estes. Dentro do KBD temos as funções *getKey()* e *waitKey()*, responsáveis por este processo, fazendo uso do *HAL* para reconhecer o código

da tecla premida no teclado *hardware*, simulado ou não, e fazendo uma correspondência ao seu carácter.

2.4 LCD

Este ficheiro define um objeto que controla o LCD através de várias funções para o iniciar, escrever dados ou comandos e manipular o cursor. A função *init()* inicializa o display, configurando-o primeiro no modo de 8 bits e depois no modo de 4 bits. As função *write(c:Char)* escreve um único carácter convertendo-o para inteiro e chamando a função *writeDATA()*. A *write(text:String)* escreve uma sequência de caracteres através da função anterior. A função *writeDATA()* chama a função *writeBYTE()* com o argumento *rs* a *true*, tal como a função *writeCMD* chama a função *writeBYTE()* com o argumento *rs* a *false*, distinguindo-se um do outro através do valor de *rs*. A função *writeByte()* escreve Bytes dividindo-os em Nibbles de 4 bits, escrevendo cada nibble separadamente. A função *writeNibble()* escreve um nibble de comando ou dados no LCD chamando a função correta dependendo do SERIALINTERFACE, seja em paralelo ou em série. Ainda não foi implementada a escrita em série. A função *writeNibbleParallel()* começa por definir o tipo de instrução que vai escrever, comando ou dados, ativa o *enable* e depois escreve o suposto comando ou dado de 4 bits, desativando o *enable* após a escrita da instrução. A função *cursor()* manda uma linha e um comando para posicionar o cursor no display. A função *clear()* envia um comando definido nas configurações do LCD que limpa o display.

2.5 TUI

Neste momento, o TUI é a nossa entidade que gere o LCD e o KBD, de forma a escrever com uma maior facilidade o que for pretendido no display. Por enquanto, foi feito uso dele de forma a testar o bom funcionamento dos outros módulos acima referidos e fazer o chamamento de instruções de uma forma mais abstracta, facilitando o uso dos outros módulos.

3 Conclusões

Concluindo, até ao dado momento, foi realizado um dado número de módulos de forma a termos uma componente em hardware, correspondente ao descodificação teclado matricial 4x4, que pretendíamos implementar e fez-se a sua ligação ao *Control* capaz de com a informação descodificada, apresentar a tecla premida no teclado no *display*. Isto mostra que tendo um *Key Decode* funcional, mesmo não tendo os outros módulos pertencentes ao *KeyBoard Reader*, podemos fazer uso dele de forma a ter o comportamento pretendido. No futuro, prevê-se a implementação dos restantes módulos *Hardware* apresentados na introdução, assim como os restantes módulos *Software* de forma a apresentar um melhor funcionamento do sistema.

A VHDL

A.1 roulette.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

— This is the top-level entity responsible for running the actual program
entity roulette is

```
    port (
        Liness: in std_logic_vector(3 downto 0);
        CLK    : in std_logic;
        Reset  : in std_logic;

        LCD_RS : out std_logic;
        LCD_EN : out std_logic;
        LCD_DATA: out std_logic_vector(7 downto 4);

        Colss : out std_logic_vector(3 downto 0);
        Kout   : out std_logic_vector(3 downto 0);
        Kval   : out std_logic;
    );
end roulette;
```

architecture structural of roulette is

```
    component Key_decode is
        port (
            Kack    : in std_logic;
            Liness  : in std_logic_vector(3 downto 0);
            CLK      : in std_logic;
            Reset   : in std_logic;

            Colss   : out std_logic_vector(3 downto 0);
            Kout     : out std_logic_vector(3 downto 0);
            Kval     : out std_logic;
        );
    end component;

    component UsbPort is
        port (
            inputPort    : IN  STD_LOGIC_VECTOR(7 DOWNTO 0);
            outputPort   : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        );
    end component;

    signal sig_k3_0 : std_logic_vector(3 downto 0);
    signal sig_kscan : std_logic_vector(1 downto 0);
```



```
signal sig_cols          : std_logic_vector(3 downto 0);
signal sig_kval          : std_logic;
```

— Valores n o atribuidos correspondentes aos bits 5–7 do input do UsbPort
— Este sinal foi criado para n o haver erros associados ao Usbport ao abrir o

```
signal inputSignal : std_logic := '0';
```

```
signal sig_d7_4      : std_logic_vector(3 downto 0);
signal sig_enable    : std_logic;
signal sig_rs        : std_logic;
```

```
signal sig_kack_outusbport : std_logic;
```

```
begin
```

```
keydecode:      Key_decode port map (
    Kack      => sig_kack_outusbport ,
    Liness    => Liness ,
    CLK       => CLK ,
    Reset     => Reset ,
    Colss     => sig_cols ,
    Kout      => sig_k3_0 ,
    Kval      => sig_kval
);
```

```
usbPortVHD:      UsbPort port map (
    inputPort(0)  => sig_kval ,
    inputPort(1)  => sig_k3_0(0) ,
    inputPort(2)  => sig_k3_0(1) ,
    inputPort(3)  => sig_k3_0(2) ,
    inputPort(4)  => sig_k3_0(3) ,

    — Valores n o atribuidos
    inputPort(5)  => inputSignal ,
    inputPort(6)  => inputSignal ,
    inputPort(7)  => inputSignal ,

    outputPort(0) => sig_kack_outusbport ,
    outputPort(1) => sig_d7_4(0) ,
    outputPort(2) => sig_d7_4(1) ,
    outputPort(3) => sig_d7_4(2) ,
    outputPort(4) => sig_d7_4(3) ,

    — Valores n o atribuidos
    outputPort(5) => inputSignal ,

    outputPort(6) => sig_rs ,
    outputPort(7) => sig_enable
```

```
);  
  
LCD_RS    <= sig_rs;  
LCD_EN    <= sig_enable;  
LCD_DATA  <= sig_d7_4;  
  
Kval      <= sig_kval;  
Kout      <= sig_k3_0;  
Colss     <= sig_cols;  
  
end structural;
```

A.2 Key_reader.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity Key_reader is
    port (
        Kack      : in std_logic;
        Liness     : in std_logic_vector(3 downto 0);
        CLK        : in std_logic;
        Reset      : in std_logic;

        Colss      : out std_logic_vector(3 downto 0);
        Kout        : out std_logic_vector(3 downto 0);
        Kval        : out std_logic
    );
end Key_reader;

architecture structural of Key_reader is

    component key_decode is
        port (
            Kack      : in std_logic;
            Liness     : in std_logic_vector(3 downto 0);
            CLK        : in std_logic;
            Reset      : in std_logic;

            Colss      : out std_logic_vector(3 downto 0);
            Kout        : out std_logic_vector(3 downto 0);
            Kval        : out std_logic
        );
    end component;

    — Sinais internos
    signal sig_kpress : std_logic;
    signal sig_k3      : std_logic_vector(3 downto 0);
    signal sig_cols    : std_logic_vector(3 downto 0);
    signal sig_kval     : std_logic;

    begin

    keydecode: key_decode port map (
        Kack  => Kack,
        Liness => Liness,
        CLK   => CLK,
        Reset => Reset,
        Colss => sig_cols,
        Kout  => sig_k3,
        Kval  => sig_kval
    );
```

```
Kval <= sig_kval;  
Kout <= sig_k3;  
Colss <= sig_cols;  
  
end structural;
```


A.3 KEY_DECODE/Key_decode.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity Key_decode is
    port (
        Kack      : in std_logic;
        Liness     : in std_logic_vector(3 downto 0);
        CLK        : in std_logic;
        Reset      : in std_logic;

        Colss      : out std_logic_vector(3 downto 0);
        Kout        : out std_logic_vector(3 downto 0);
        Kval        : out std_logic
    );
end Key_decode;

architecture structural of Key_decode is

    component key_scanner is
        port (
            KScan : in std_logic_vector(1 downto 0);
            lines  : in std_logic_vector(3 downto 0);
            CLK    : in std_logic;
            Reset  : in std_logic;

            columns : out std_logic_vector(3 downto 0);
            KPress  : out std_logic;
            K       : out std_logic_vector(3 downto 0)
        );
    end component;

    component KeyControl is
        port (
            reset      : in std_logic;
            clk        : in std_logic;
            Kpress     : in std_logic;
            Kack       : in std_logic;

            KScan      : out std_logic_vector(1 downto 0);
            Kval       : out std_logic
        );
    end component;

    signal sig_kpress : std_logic;
    signal sig_k3      : std_logic_vector(3 downto 0);
    signal sig_kscan   : std_logic_vector(1 downto 0);
    signal sig_cols    : std_logic_vector(3 downto 0);

```

```
signal sig_kval          : std_logic;

begin

keyscan: key_scanner port map (
    KScan  => sig_kscan ,
    lines  => Lines ,
    CLK    => CLK,
    Reset  => Reset ,
    columns => sig_cols ,
    KPress => sig_kpress ,
    K      => sig_k3
);

keycontrols: KeyControl port map (
    reset  => Reset ,
    clk    => CLK,
    Kpress => sig_kpress ,
    Kack   => Kack ,
    KScan  => sig_kscan ,
    Kval   => sig_kval
);

Kval <= sig_kval;
Kout <= sig_k3;
Colss <= sig_cols;

end structural;
```

A.4 KEY_DECODE/KeyControl/KeyControl.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

— This is the entity is the state machine that controls the keydecode file
 entity KeyControl is

```
    port (
        reset           : in std_logic;
        clk             : in std_logic;
        Kpress          : in std_logic;
        Kack             : in std_logic;

        KScan           : out std_logic_vector(1 downto 0);
        Kval             : out std_logic
    );
```

```
end KeyControl;
```

architecture behavioral of KeyControl is

```
type STATE_TYPE is (State_Scan_Columns, State_Scan_Lines, State_Val, State_Ack_Waiting);
```

```
signal CurrentState, NextState: STATE_TYPE;
```

```
begin
```

— Flip-Flop's

```
CurrentState <= State_Scan_Columns when RESET = '1' else NextState when rising_edge(clk);
```

— Generate Next State

```
GenerateNextState:
```

```
process (CurrentState, Kpress, Kack)
```

```
begin
```

```
case CurrentState is
```

```
    when State_Scan_Columns => if (Kpress = '1') then
                                NextState <= State_Scan_Lines;
                                else
                                NextState <= State_Scan_Columns;
                                end if;

    when State_Scan_Lines   => NextState <= State_Val;

    when State_Val          => if (Kack = '1' and Kpress = '0') then
                                NextState <= State_Ack_Waiting;
                                else
                                NextState <= State_Val;
                                end if;
```

```
when State_Ack_Waiting =>
    if (Kack = '0') then
        NextState <= State_Scan_Columns;
    else
        NextState <= State_Ack_Waiting;
    end if;

end case;
end process;

-- Generate outputs

KScan(0) <= '1' when (CurrentState = State_Scan_Columns and Kpress = '0') else
KScan(1) <= '1' when (CurrentState = State_Scan_Lines) else '0';
Kval <= '1' when (CurrentState = State_Val) else '0';

end behavioral;
```

A.5 KEY_DECODE/KEY_SCANNER/key_scanner.vhd

```
library ieee;
use ieee.std_logic_1164.all;
```

— This entity defines the key scanner circuit
entity key_scanner is

```
    port (
        KScan    : in std_logic_vector(1 downto 0);
        lines    : in std_logic_vector(3 downto 0);
        CLK      : in std_logic;
        Reset     : in std_logic;

        columns  : out std_logic_vector(3 downto 0);
        KPress   : out std_logic;
        K        : out std_logic_vector(3 downto 0)
    );
```

```
end key_scanner;
```

architecture structural of key_scanner is

```
    component counter is
        port (
            CE          : in std_logic;
            CLK         : in std_logic;
            reset       : in std_logic;

            parallel_load_flag : in std_logic;
            parallel_load_value : in std_logic_vector(1 downto 0);

            count : out std_logic_vector(1 downto 0)
        );
    end component;

    component decoder_2x4 is
        port (
            S : in std_logic_vector (1 downto 0);
            Y : out std_logic_vector (3 downto 0)
        );
    end component;

    component priority_encoder is
        port (
            A      : in std_logic_vector(3 downto 0);

            Y      : out std_logic_vector(1 downto 0);
            GS     : out std_logic
```

```
    );
end component;

component register_2bits is
    port (
        CLK    : in  std_logic;
        RESET  : in  std_logic;
        SET    : in  std_logic;
        D      : in  std_logic_vector(1 downto 0);
        EN     : in  std_logic;
        Q      : out std_logic_vector(1 downto 0)
    );
end component;

signal counter_to_decoder: std_logic_vector(1 downto 0);
signal penc_to_reg      : std_logic_vector(1 downto 0);
signal cols              : std_logic_vector(3 downto 0);
signal penc_to_kpress   : std_logic;
signal K_low            : std_logic_vector(1 downto 0);
signal lines_signal     : std_logic_vector(3 downto 0);

begin

Contador: counter port map (
    CE => KScan(0),
    CLK => CLK,
    reset => Reset,
    parallel_load_flag => '0',
    parallel_load_value => "01",
    count => counter_to_decoder
);

Decoder: decoder_2x4 port map (
    S => counter_to_decoder,
    Y(0) => cols(0),
    Y(1) => cols(1),
    Y(2) => cols(2),
    Y(3) => cols(3)
);

lines_signal <= not lines;

Penc: priority_encoder port map (
    A(0) => lines_signal(0),
    A(1) => lines_signal(1),
    A(2) => lines_signal(2),
    A(3) => lines_signal(3),
```

```
        Y => penc_to_reg ,
        GS => penc_to_kpress
    );

    Reg: register_2bits port map (
        CLK      => KScan(1),
        RESET    => Reset ,
        SET      => '0' ,
        D        => penc_to_reg ,
        EN       => '1' ,
        Q        => K_low
    );

    K(3) <= counter_to_decoder(1);
    K(2) <= counter_to_decoder(0);
    K(1) <= K_low(1);
    K(0) <= K_low(0);
    columns <= not cols;
    KPress <= penc_to_kpress;

end structural;
```

A.6 KEY_DECODE/KEY_SCANNER/COUNTER/counter.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity counter is
    port (
        CE      : in std_logic;
        CLK     : in std_logic;
        reset    : in std_logic;

        parallel_load_flag : in std_logic;
        parallel_load_value : in std_logic_vector(1 downto 0);

        count : out std_logic_vector(1 downto 0)
    );
end counter;

architecture behavioral of counter is

    component adder_2bits is
        port (
            A : in std_logic_vector(1 downto 0);
            B : in std_logic_vector(1 downto 0);

            carry_in : in std_logic;
            carry_out : out std_logic;

            result : out std_logic_vector(1 downto 0)
        );
    end component;

    component mux_2x1 is
        port (
            A : in std_logic_vector(1 downto 0);
            B : in std_logic_vector(1 downto 0);

            selector : in std_logic;

            result : out std_logic_vector(1 downto 0)
        );
    end component;
```

```
end component;
```

— Imports the 2bit registry
component register_2bits is

```
    port (
CLK      : in  std_logic;
RESET    : in  std_logic;
SET       : in  std_logic;
D         : in  std_logic_vector(1 downto 0);
EN        : in  std_logic;
Q         : out std_logic_vector(1 downto 0)
    );

end component;
```

— The carry out signal for the 2 bit adder
signal carry_out_adder_2bits : std_logic_vector(1 downto 0);
signal result_adder_2bits : std_logic_vector(1 downto 0);
signal result_mux : std_logic_vector(1 downto 0);
signal result_register_2bits : std_logic_vector(1 downto 0);

begin

— Instantiates the 2 bit adder that always adds 1
instance_adder_2bits : adder_2bits

```
    port map (
        A => result_register_2bits ,
        B => "01",
        carry_in => '0',
        carry_out => open ,

        result => result_adder_2bits
    );
```

— Instantiates the MUX
instance_mux_2x1 : mux_2x1

```
    port map (
        A => result_adder_2bits ,
        B => parallel_load_value ,

        selector => parallel_load_flag ,
        result    => result_mux
    );
```

```
— Instantiates the 4 bit register
instance_registry_2bits : register_2bits

    port map (
        CLK    => CLK,
        RESET  => reset ,
        SET    => '1',
        D      => result_mux ,
        EN     => CE,
        Q      => result_register_2bits
    );

count <= result_register_2bits;

end behavioral;
```

A.7 KEY_DECODE/KEY_SCANNER/COUNTER/adder_2bits.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity adder_2bits is
    port (
        A : in std_logic_vector(1 downto 0);
        B : in std_logic_vector(1 downto 0);

        carry_in  : in std_logic;
        carry_out  : out std_logic;

        result : out std_logic_vector(1 downto 0)
    );
end adder_2bits;

architecture behavioral of adder_2bits is
    — Imports the full adder from the specification in the full_adder entity
    component full_adder
        port (
            A : in std_logic;
            B : in std_logic;

            carry_in  : in std_logic;
            carry_out  : out std_logic;

            result : out std_logic
        );
    end component;

    — Declares the output and carry variables for the 4 full adders
    signal out_full_adder_1 : std_logic;
    signal out_full_adder_2 : std_logic;

    signal carry_full_adder_1 : std_logic;
    signal carry_full_adder_2 : std_logic;

begin
    — Instantiates a full adder with all the default values
    instance_full_adder_1 : full_adder
```

```
        port map (
            A => A(0),
            B => B(0),

            carry_in  => carry_in ,
            carry_out => carry_full_adder_1 ,

            result => out_full_adder_1
        );

-- Instantiates three more full adders with the previous carries as inputs
-- and with incremental bit placements for the A and B inputs
instance_full_adder_2 : full_adder

        port map (
            A => A(1),
            B => B(1),

            carry_in  => carry_full_adder_1 ,
            carry_out => carry_full_adder_2 ,

            result => out_full_adder_2
        );

-- Defines the adder/subtractor's carry out as the last full adder's carry
carry_out <= carry_full_adder_2;

-- Sets the result bits in order
result(0) <= out_full_adder_1;
result(1) <= out_full_adder_2;

end behavioral;
```

A.8 KEY_DECODE/KEY_SCANNER/COUNTER/FFD.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

— Entity declaration for D Flip–Flop with enable, reset, and set functionalities

```
ENTITY FFD IS
    PORT (
        CLK      : IN    std_logic;    — Clock input
        RESET    : IN    std_logic;    — Asynchronous reset input (active high)
        SET      : IN    std_logic;    — Asynchronous set input (active high)
        D        : IN    std_logic;    — Data input
        EN       : IN    std_logic;    — Enable input (active high)
        Q        : OUT   std_logic     — Data output
    );
END FFD;
```

— Architecture describing the behavior of the Flip–Flop

```
ARCHITECTURE logicFunction OF FFD IS
BEGIN
```

— Conditional signal assignment with priority: RESET > SET > ENABLE

```
Q <= '0' WHEN RESET = '1' ELSE           — Priority 1: Reset is active, set Q to '0'
    '1' WHEN SET = '1' ELSE               — Priority 2: Set is active, set Q to '1'
    D WHEN rising_edge(CLK) AND EN = '1'; — Priority 3: Enable is active, update Q
```

```
END logicFunction;
```

A.9 KEY_DECODE/KEY_SCANNER/COUNTER/full_adder.vhd

```
library ieee;  
use ieee.std_logic_1164.all;
```

— This entity is responsible for acting as a full adder, using two half-adders
— in succession to account for first bit carries
entity full_adder is

```
    port (  
        A : in std_logic;  
        B : in std_logic;  
  
        carry_in  : in std_logic;  
        carry_out : out std_logic;  
  
        result : out std_logic  
    );
```

```
end full_adder;
```

architecture behavioral of full_adder is

— Imports the half adder from the specification in the half_adder entity
component half_adder

```
    port (  
        A : in std_logic;  
        B : in std_logic;  
  
        result      : out std_logic;  
        carry_out   : out std_logic  
    );
```

```
end component;
```

— Initialises the result carriers for the half-adders

```
signal out_half_adder_1 : std_logic;  
signal out_half_adder_2 : std_logic;  
  
signal carry_half_adder_1 : std_logic;  
signal carry_half_adder_2 : std_logic;
```

```
begin
```

— Instantiate the first half adder with the full adder's A and B
instance_half_adder_1 : half_adder

```
port map (
    A => A,
    B => B,

    result => out_half_adder_1,
    carry_out => carry_half_adder_1
);

-- Instantiate the second half adder with the first half adder's result and
-- carry, to account for the bit carry
instance_half_adder_2: half_adder

port map (
    A => out_half_adder_1,
    B => carry_in,

    result => out_half_adder_2,
    carry_out => carry_half_adder_2
);

result <= out_half_adder_2;
carry_out <= (carry_half_adder_1 or carry_half_adder_2);

end behavioral;
```

A.10 KEY_DECODE/KEY_SCANNER/COUNTER/half_adder.vhd

```
library ieee;
use ieee.std_logic_1164.all;

— This entity is responsible for acting as a half adder, simply XOR'ing two
— to sum them returning their value and carry.
entity half_adder is

    port (
        A : in std_logic;
        B : in std_logic;

        result      : out std_logic;
        carry_out   : out std_logic
    );

end half_adder;

architecture structural of half_adder is
begin

    result      <= A xor B;
    carry_out   <= A and B;

end structural;
```

A.11 KEY_DECODE/KEY_SCANNER/COUNTER/MUX2x1.vhd

```
library ieee;
use ieee.std_logic_1164.all;

— This entity is responsible for acting like a MUX, and giving the output based
— on the selected inputs
entity mux_2x1 is

    port (
        A : in std_logic_vector(1 downto 0);
        B : in std_logic_vector(1 downto 0);

        selector : in std_logic;

        result : out std_logic_vector(1 downto 0)
    );

end mux_2x1;

— Implements the logic of a MUX with two inputs and one selector
architecture structural of mux_2x1 is
begin

    result(1) <= (A(1) and not selector) or (B(1) and selector);
    result(0) <= (A(0) and not selector) or (B(0) and selector);

end structural;
```

A.12 KEY_DECODE/KEY_SCANNER/COUNTER/registry_2bits.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity register_2bits is

    port (
        CLK      : in  std_logic;
        RESET    : in  std_logic;
        SET       : in  std_logic;
        D         : in  std_logic_vector(1 downto 0);
        EN        : in  std_logic;
        Q         : out std_logic_vector(1 downto 0)
    );

end register_2bits;

architecture behavioral of register_2bits is

    — Declare the component for the flip–flop (FFD)
    component FFD is

        port (
            CLK      : in  std_logic;
            RESET    : in  std_logic;
            SET       : in  std_logic;
            D         : in  std_logic;
            EN        : in  std_logic;
            Q         : out std_logic
        );

    end component;

begin

    — Instantiate the flip–flops (FFD) for each bit of the data input
    FFD1: FFD
        port map (
            CLK      => CLK,
            RESET    => RESET,
            SET       => '0',
            EN        => EN,
            D         => D(0),
            Q         => Q(0)
        );

    FFD2: FFD
        port map (
```

```
        CLK    => CLK,  
        RESET => RESET,  
        SET    => '0',  
        EN     => EN,  
        D      => D(1),  
        Q      => Q(1)  
    );  
  
end behavioral;
```

A.13 KEY_DECODE/KEY_SCANNER/COUNTER/registry_2bits_counter.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity register_2bits_counter is

    port (
        CLK      : in  std_logic;
        RESET    : in  std_logic;
        SET       : in  std_logic;
        D         : in  std_logic_vector(1 downto 0);
        EN        : in  std_logic;
        Q         : out std_logic_vector(1 downto 0)
    );

end register_2bits_counter;
```

architecture behavioral of register_2bits_counter is

— Declare the component for the flip–flop (FFD)
component FFD is

```
    port (
        CLK      : in  std_logic;
        RESET    : in  std_logic;
        SET       : in  std_logic;
        D         : in  std_logic;
        EN        : in  std_logic;
        Q         : out std_logic
    );

end component;
```

begin

— Instantiate the flip–flops (FFD) for each bit of the data input

FFD1: FFD

```
    port map (
        CLK      => CLK,
        RESET    => RESET,
        SET      => '0',
        EN        => EN,
        D        => D(0),
        Q        => Q(0)
    );
```

FFD2: FFD

```
    port map (
```

```
        CLK    => CLK,  
        RESET => RESET,  
        SET    => '0',  
        EN     => EN,  
        D      => D(1),  
        Q      => Q(1)  
    );  
  
end behavioral;
```

A.14 KEY_DECODE/KEY_SCANNER/DEC/decoder_2x4.vhd

```
library ieee;
use ieee.std_logic_1164.all;

— This entity is responsible for acting as a 2x4 decoder
entity decoder_2x4 is

    port(
        S : in std_logic_vector (1 downto 0);
        Y : out std_logic_vector (3 downto 0)
    );

end decoder_2x4;

architecture structural of decoder_2x4 is
begin

    Y(0) <= (not S(1) and not S(0));
    Y(1) <= (not S(1) and S(0));
    Y(2) <= (S(1) and not S(0));
    Y(3) <= (S(1) and S(0));

end structural;
```

A.15 KEY_DECODE/KEY_SCANNER/PENC/mux_2x1_penc.vhd

```
library ieee;  
use ieee.std_logic_1164.all;
```

— This entity is responsible for acting like a MUX, and giving the output based
— on the selected inputs
entity mux_2x1_penc is

```
    port (  
        A : in std_logic;  
        B : in std_logic;  
  
        selector : in std_logic;  
  
        result : out std_logic  
    );
```

```
end mux_2x1_penc;
```

— Implements the logic of a MUX with two inputs and one selector
architecture structural of mux_2x1_penc is
begin

```
    result <= (A and not selector) or (B and selector);
```

```
end structural;
```

A.16 KEY_DECODE/KEY_SCANNER/PENC/partial_priority_encoder.vhd

```
LIBRARY ieee;
Use ieee.std_logic_1164.all;

— This entity is responsible for corresponding the 4 bits of the inputs to 2 bits
— with Y(0) being A(0) and A(1) and Y(1) being the A(2) and A(3)
— Gs is a signal that will be on when one of the inputs is active
entity partial_priority_encoder is
    port(
        A      : in std_logic_vector(1 downto 0);

        Y      : out std_logic;
        GS     : out std_logic
    );
end partial_priority_encoder;

architecture structural of partial_priority_encoder is

begin

    Y <= not A(0);
    GS <= A(0) or A(1);

end structural;
```


A.17 KEY_DECODE/KEY_SCANNER/PENC/priority_encoder.vhd

```

LIBRARY ieee;
Use ieee.std_logic_1164.all;

— This entity is responsible for corresponding the 4 bits of the inputs to 2 bits
— with Y(0) being A(0) and A(1) and Y(1) being the A(2) and A(3)
— Gs is a signal that will be on when one of the inputs is active
entity priority_encoder is
    port(
        A      : in std_logic_vector(3 downto 0);

        Y      : out std_logic_vector(1 downto 0);
        GS     : out std_logic
    );
end priority_encoder;

architecture structural of priority_encoder is

    component partial_priority_encoder is
        port(
            A      : in std_logic_vector(1 downto 0);

            Y      : out std_logic;
            GS     : out std_logic
        );
    end component;

    component mux_2x1_penc is
        port (
            A : in std_logic;
            B : in std_logic;

            selector : in std_logic;

            result : out std_logic
        );
    end component;

    signal Y_PPenc1 : std_logic;
    signal GS_PPenc1 : std_logic;

    signal Y_PPenc2 : std_logic;
    signal GS_PPenc2 : std_logic;

    signal Y_PPenc3 : std_logic;
    signal GS_PPenc3 : std_logic;

```

```

    signal out_mux2x1 : std_logic;

begin

    Pencil1: partial_priority_encoder
    port map(
        A(0) => A(0) ,
        A(1) => A(1) ,

        Y      => Y_PPencil1,
        GS     => GS_PPencil1
    );

    Pencil2: partial_priority_encoder
    port map(
        A(0) => A(2) ,
        A(1) => A(3) ,

        Y      => Y_PPencil2,
        GS     => GS_PPencil2
    );

    Pencil3: partial_priority_encoder
    port map(
        A(0) => GS_PPencil1,
        A(1) => GS_PPencil2,

        Y      => Y_PPencil3,
        GS     => GS_PPencil3
    );

    Mux2x1: mux_2x1_penc
    port map(
        A      => Y_PPencil1,
        B      => Y_PPencil2,

        selector => Y_PPencil3,
        result  => out_mux2x1
    );

    -- Saída do Pencil

    Y(0)  <= out_mux2x1;
    Y(1)  <= Y_PPencil3;

    GS    <= GS_PPencil3;

end structural;

```

A.18 UsbPort.vhd

```

— Copyright (C) 2020 Intel Corporation. All rights reserved.
— Your use of Intel Corporation's design tools, logic functions
— and other software and tools, and any partner logic
— functions, and any output files from any of the foregoing
— (including device programming or simulation files), and any
— associated documentation or information are expressly subject
— to the terms and conditions of the Intel Program License
— Subscription Agreement, the Intel Quartus Prime License Agreement,
— the Intel FPGA IP License Agreement, or other applicable license
— agreement, including, without limitation, that your use is for
— the sole purpose of programming logic devices manufactured by
— Intel and sold by Intel or its authorized distributors. Please
— refer to the applicable agreement for further details, at
— https://fpgasoftware.intel.com/eula.

— PROGRAM "Quartus Prime"
— VERSION "Version 20.1.1 Build 720 11/11/2020 SJ Lite Edition"
— CREATED "Tue Mar 01 09:42:31 2022"

LIBRARY ieee;
USE ieee.std_logic_1164.all;

LIBRARY work;

ENTITY UsbPort IS
    PORT
    (
        inputPort: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        outputPort : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
END UsbPort;

ARCHITECTURE bdf_type OF UsbPort IS

    COMPONENT sld_virtual_jtag
    GENERIC (lpm_type : STRING;
            sld_auto_instance_index : STRING;
            sld_instance_index : INTEGER;
            sld_ir_width : INTEGER;
            sld_sim_action : STRING;
            sld_sim_n_scan : INTEGER;
            sld_sim_total_length : INTEGER
            );
    PORT(tdo : IN STD_LOGIC;
        ir_out : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        tck : OUT STD_LOGIC;
        tdi : OUT STD_LOGIC;
        virtual_state_cdr : OUT STD_LOGIC;

```

```

        virtual_state_sdr : OUT STD_LOGIC;
        virtual_state_e1dr : OUT STD_LOGIC;
        virtual_state_pdr : OUT STD_LOGIC;
        virtual_state_e2dr : OUT STD_LOGIC;
        virtual_state_udr : OUT STD_LOGIC;
        virtual_state_cir : OUT STD_LOGIC;
        virtual_state_uir : OUT STD_LOGIC;
        tms : OUT STD_LOGIC;
        jtag_state_tlr : OUT STD_LOGIC;
        jtag_state_rti : OUT STD_LOGIC;
        jtag_state_sdrs : OUT STD_LOGIC;
        jtag_state_cdr : OUT STD_LOGIC;
        jtag_state_sdr : OUT STD_LOGIC;
        jtag_state_e1dr : OUT STD_LOGIC;
        jtag_state_pdr : OUT STD_LOGIC;
        jtag_state_e2dr : OUT STD_LOGIC;
        jtag_state_udr : OUT STD_LOGIC;
        jtag_state_sirs : OUT STD_LOGIC;
        jtag_state_cir : OUT STD_LOGIC;
        jtag_state_sir : OUT STD_LOGIC;
        jtag_state_elir : OUT STD_LOGIC;
        jtag_state_pir : OUT STD_LOGIC;
        jtag_state_e2ir : OUT STD_LOGIC;
        jtag_state_uir : OUT STD_LOGIC;
        ir_in : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
END COMPONENT;

BEGIN

b2v_inst : sld_virtual_jtag
GENERIC MAP(lpm_type => "sld_virtual_jtag",
            sld_auto_instance_index => "YES",
            sld_instance_index => 0,
            sld_ir_width => 8,
            sld_sim_action => "UNUSED",
            sld_sim_n_scan => 0,
            sld_sim_total_length => 0
        )
PORT MAP(ir_out => inputPort ,
        ir_in => outputPort);

END bdf_type;
```

B TestBench

B.1 testbench/Key_reader_tb.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity Key_reader_tb is
end Key_reader_tb;

architecture behavioral of Key_reader_tb is

    component Key_reader is
        port (
            Kack      : in std_logic;
            Liness     : in std_logic_vector(3 downto 0);
            CLK        : in std_logic;
            Reset      : in std_logic;
            Colss      : out std_logic_vector(3 downto 0);
            Kout       : out std_logic_vector(3 downto 0);
            Kval       : out std_logic
        );
    end component;

    constant clk_period      : TIME := 10 ns;
    constant half_clk_period : TIME := clk_period / 2;

    signal Kack_tb      : std_logic;
    signal lines_tb     : std_logic_vector(3 downto 0);
    signal clk_tb       : std_logic;
    signal reset_tb     : std_logic;
    signal columns_tb   : std_logic_vector(3 downto 0);
    signal K_tb         : std_logic_vector(3 downto 0);
    signal Kval_tb      : std_logic;

begin

    UUT : Key_reader
        port map (
            Kack  => Kack_tb,
            Liness => lines_tb,
            CLK   => clk_tb,
            Reset => reset_tb,
            Colss => columns_tb,
            Kout  => K_tb,
            Kval  => Kval_tb
        );

    clk_gen: process
    begin
        reset_tb <= '1';
        lines_tb <= "1111";
```



```
Kack_tb <= '0';
wait for clk_period;

lines_tb <= "1111"; — not Kpress
reset_tb <= '0';
  Kack_tb <= '1';
wait for clk_period * 2;

— Test of first line
lines_tb <= "0111";
wait for clk_period * 2;

Kack_tb <= '1';
wait for clk_period * 2;

lines_tb <= "1111"; — not Kpress
wait for clk_period * 2;

Kack_tb <= '0';
wait for clk_period * 2;

— Test of second line
lines_tb <= "1011";
wait for clk_period * 2;

Kack_tb <= '1';
wait for clk_period * 2;

lines_tb <= "1111"; — not Kpress
wait for clk_period * 2;

Kack_tb <= '0';
wait for clk_period * 2;

— Test of third line
lines_tb <= "1101";
wait for clk_period * 2;

Kack_tb <= '1';
wait for clk_period * 2;

lines_tb <= "1111"; — not Kpress
wait for clk_period * 2;

Kack_tb <= '0';
wait for clk_period * 2;

— Test of fourth line
lines_tb <= "1110";
wait for clk_period * 2;
```

```
Kack_tb <= '1';  
wait for clk_period * 2;  
  
lines_tb <= "1111"; — not Kpress  
wait for clk_period * 2;  
  
Kack_tb <= '0';  
wait for clk_period * 2;  
  
wait;  
end process;  
  
end behavioral;
```

B.2 testbench/Key_decode_tb.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity Key_decode_tb is
end Key_decode_tb;

architecture behavioral of Key_decode_tb is

    component Key_decode is
        port (
            Kack    : in std_logic;
            Liness  : in std_logic_vector(3 downto 0);
            CLK     : in std_logic;
            Reset   : in std_logic;

            Colss   : out std_logic_vector(3 downto 0);
            Kout    : out std_logic_vector(3 downto 0);
            Kval    : out std_logic
        );
    end component;

    constant clk_period      : TIME := 20 ns;
    constant half_clk_period : TIME := clk_period / 2;

    signal Kack_tb      : std_logic;
    signal lines_tb     : std_logic_vector(3 downto 0);
    signal clk_tb       : std_logic;
    signal reset_tb     : std_logic;
    signal columns_tb   : std_logic_vector(3 downto 0);
    signal K_tb         : std_logic_vector(3 downto 0);
    signal Kval_tb      : std_logic;

begin

    UUT : Key_decode
        port map (
            Kack    => Kack_tb,
            Liness  => lines_tb,
            CLK     => clk_tb,
            Reset   => reset_tb,
            Colss   => columns_tb,
            Kval    => Kval_tb,
            Kout    => K_tb
        );

    clk_gen: process
    begin
        clk_tb <= '0';
```

```
        wait for half_clk_period;
        clk_tb <= '1';
        wait for half_clk_period;
    end process;

stimulus: process
begin
    reset_tb <= '1';
    lines_tb <= "1111";
    Kack_tb <= '0';
    wait for clk_period;

    lines_tb <= "1111"; — not Kpress
    reset_tb <= '0';
    Kack_tb <= '1';
    wait for clk_period * 2;

    — Test of first line
    lines_tb <= "0111";
    wait for clk_period * 2;

    Kack_tb <= '1';
    wait for clk_period * 2;

    lines_tb <= "1111"; — not Kpress
    wait for clk_period * 2;

    Kack_tb <= '0';
    wait for clk_period * 2;

    — Test of second line
    lines_tb <= "1011";
    wait for clk_period * 2;

    Kack_tb <= '1';
    wait for clk_period * 2;

    lines_tb <= "1111"; — not Kpress
    wait for clk_period * 2;

    Kack_tb <= '0';
    wait for clk_period * 2;

    — Test of third line
    lines_tb <= "1101";
    wait for clk_period * 2;

    Kack_tb <= '1';
    wait for clk_period * 2;
```

```
lines_tb <= "1111"; — not Kpress
wait for clk_period * 2;

Kack_tb <= '0';
wait for clk_period * 2;

— Test of fourth line
lines_tb <= "1110";
wait for clk_period * 2;

Kack_tb <= '1';
wait for clk_period * 2;

lines_tb <= "1111"; — not Kpress
wait for clk_period * 2;

Kack_tb <= '0';
wait for clk_period * 2;

wait;
end process;

end behavioral;
```

B.3 testbench/KeyControl_tb.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity KeyControl_tb is
end KeyControl_tb;

architecture behavioral of KeyControl_tb is

    component KeyControl is
        port (
            reset    : in std_logic;
            clk      : in std_logic;
            Kpress   : in std_logic;
            Kack      : in std_logic;

            KScan    : out std_logic_vector(1 downto 0);
            Kval      : out std_logic
        );
    end component;

    constant clk_period      : TIME := 10 ns;
    constant half_clk_period : TIME := clk_period / 2;

    signal reset_tb    : std_logic;
    signal clk_tb      : std_logic;
    signal Kpress_tb   : std_logic;
    signal Kack_tb     : std_logic;
    signal KScan_tb    : std_logic_vector(1 downto 0);
    signal Kval_tb     : std_logic;

begin

    UUT : KeyControl
        port map (
            reset => reset_tb,
            clk   => clk_tb,
            Kpress => Kpress_tb,
            Kack   => Kack_tb,
            KScan  => KScan_tb,
            Kval   => Kval_tb
        );

    clk_gen: process
    begin
        clk_tb <= '0';
        wait for half_clk_period;
        clk_tb <= '1';
        wait for half_clk_period;
```

```
end process ;

stimulus: process
begin
    reset_tb    <= '1';
    wait for clk_period;

    Kpress_tb    <= '0';
    Kack_tb      <= '0';
    reset_tb     <= '0';
    wait for clk_period;

    Kpress_tb    <= '1';
    Kack_tb      <= '0';
    wait for clk_period * 2;

    Kpress_tb    <= '0';
    Kack_tb      <= '0';
    wait for clk_period;

    Kpress_tb    <= '1';
    Kack_tb      <= '1';
    wait for clk_period;

    Kpress_tb    <= '1';
    Kack_tb      <= '0';
    wait for clk_period;

    Kpress_tb    <= '0';
    Kack_tb      <= '1';
    wait for clk_period;

    Kpress_tb    <= '1';
    Kack_tb      <= '1';
    wait for clk_period;

    Kpress_tb    <= '0';
    Kack_tb      <= '0';
    wait for clk_period * 2;

    wait;
end process;

end behavioral;
```

B.4 testbench/KeyScannerTb.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity Key_Scanner_tb is
end Key_Scanner_tb;

architecture behavioral of Key_Scanner_tb is

    component key_scanner is
        port(
            KScan    : in std_logic_vector(1 downto 0);
            lines    : in std_logic_vector(3 downto 0);
            CLK      : in std_logic;
            reset    : in std_logic;

            columns  : out std_logic_vector(3 downto 0);
            Kpress   : out std_logic;
            K        : out std_logic_vector(3 downto 0)
        );
    end component;

    constant clk_period      : TIME := 10 ns;
    constant half_clk_period : TIME := clk_period / 2;

    signal Kscan_tb    : std_logic_vector(1 downto 0);
    signal lines_tb    : std_logic_vector(3 downto 0);
    signal clk_tb      : std_logic;
    signal reset_tb    : std_logic;
    signal columns_tb  : std_logic_vector(3 downto 0);
    signal Kpress_tb   : std_logic;
    signal K_tb        : std_logic_vector(3 downto 0);

begin

    UUT : key_scanner
        port map (
            Kscan    => Kscan_tb,
            lines    => lines_tb,
            CLK      => clk_tb,
            reset    => reset_tb,
            columns  => columns_tb,
            Kpress   => Kpress_tb,
            K        => K_tb
        );

    clk_gen: process
    begin
        clk_tb <= '0';
```

```
        wait for half_clk_period;  
        clk_tb <= '1';  
        wait for half_clk_period;  
end process;
```

```
stimulus: process  
begin
```

```
    reset_tb <= '1';  
    Kscan_tb <= "11";  
    lines_tb <= "0000";  
    wait for clk_period*2;
```

```
    reset_tb <= '0';  
    Kscan_tb <= "11";  
    lines_tb <= "0001";  
    wait for clk_period*2;
```

```
    Kscan_tb <= "10";  
    lines_tb <= "0001";  
    wait for clk_period*2;
```

```
    Kscan_tb <= "00";  
    lines_tb <= "0001";  
    wait for clk_period*2;
```

```
    Kscan_tb <= "11";  
    lines_tb <= "0010";  
    wait for clk_period*2;
```

```
    Kscan_tb <= "10";  
    lines_tb <= "0010";  
    wait for clk_period*2;
```

```
    Kscan_tb <= "00";  
    lines_tb <= "0010";  
    wait for clk_period*2;
```

```
    Kscan_tb <= "11";  
    lines_tb <= "0100";  
    wait for clk_period*2;
```

```
    Kscan_tb <= "10";  
    lines_tb <= "0100";  
    wait for clk_period*2;
```

```
    Kscan_tb <= "00";  
    lines_tb <= "0100";  
    wait for clk_period*2;
```

```
        Kscan_tb <= "11";  
        lines_tb <= "1000";  
        wait for clk_period*2;  
  
        Kscan_tb <= "10";  
        lines_tb <= "1000";  
        wait for clk_period*2;  
  
        Kscan_tb <= "00";  
        lines_tb <= "1000";  
        wait for clk_period*2;  
  
        Kscan_tb <= "11";  
        lines_tb <= "0000";  
        wait for clk_period*2;  
  
        Kscan_tb <= "10";  
        lines_tb <= "0000";  
        wait for clk_period*2;  
  
        Kscan_tb <= "00";  
        lines_tb <= "0000";  
        wait for clk_period*2;  
  
        wait;  
    end process;  
  
end behavioral;
```


B.5 testbench/CounterTb.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity counter_tb is
end counter_tb;

architecture behavioral of counter_tb is

    component counter is
        port (
            CE                : in std_logic;
            CLK                : in std_logic;
            reset              : in std_logic;
            parallel_load_flag : in std_logic;
            parallel_load_value : in std_logic_vector(1 downto 0);
            count              : out std_logic_vector(1 downto 0)
        );
    end component;

    constant clk_period      : TIME := 10 ns;
    constant half_clk_period : TIME := clk_period / 2;

    signal CE_tb                : std_logic;
    signal CLK_tb               : std_logic;
    signal reset_tb             : std_logic;
    signal parallel_load_flag_tb : std_logic;
    signal parallel_load_value_tb : std_logic_vector(1 downto 0);
    signal count_tb             : std_logic_vector(1 downto 0);

begin

    UUT: counter
        port map (
            CE                => CE_tb,
            CLK               => CLK_tb,
            reset              => reset_tb,
            parallel_load_flag => parallel_load_flag_tb,
            parallel_load_value => parallel_load_value_tb,
            count              => count_tb
        );

    — Clock Generation
    clk_gen: process
    begin
        while true loop
            CLK_tb <= '0';
            wait for half_clk_period;
        end loop
    end process
end architecture;
```

```

        CLK_tb <= '1';
        wait for half_clk_period;
    end loop;
end process;

-- Stimulus Process
stimulus: process
begin
    -- Reset the counter and enable counting
    reset_tb <= '1';
    CE_tb <= '1';
    -- Signal to use on mux that selects the parallel load
    parallel_load_flag_tb <= '0';
    -- Value that will be input in the register if the selector is 1
    parallel_load_value_tb <= "01";
    wait for clk_period;

    reset_tb <= '0';
    wait for clk_period*8;

    parallel_load_flag_tb <= '1';
    wait for clk_period*2;

    -- Stop the increment of the counter by changing the mux signal
    parallel_load_flag_tb <= '1';
    parallel_load_value_tb <= "10";

    wait for clk_period;
    wait for clk_period;

    -- Change it to the default form of the counter, increment +1
    parallel_load_flag_tb <= '0';
    parallel_load_value_tb <= "01";

    wait for clk_period*8;

    -- Disable counting
    CE_tb <= '0';
    wait for clk_period;

    wait;
end process;

end behavioral;
```

B.6 testbench/decoder_tb.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity decoder_tb is
end decoder_tb;

architecture behavioral of decoder_tb is

    component decoder_2x4 is
        port (
            S : in std_logic_vector (1 downto 0);
            Y : out std_logic_vector (3 downto 0)
        );
    end component;

    signal s_tb      : std_logic_vector(1 downto 0);
    signal y_tb      : std_logic_vector(3 downto 0);

begin

    UUT : decoder_2x4
        port map (
            S  => s_tb,
            Y  => y_tb
        );

    stimulus: process
    begin
        s_tb    <= "00";
        wait for 20 ns;

        s_tb    <= "01";
        wait for 20 ns;

        s_tb    <= "10";
        wait for 20 ns;

        s_tb    <= "11";
        wait for 20 ns;

        wait;
    end process;

end behavioral;
```

B.7 testbench/priority_encoder_tb.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity priority_encoder_tb is
end priority_encoder_tb;

architecture behavioral of priority_encoder_tb is

    component priority_encoder is
        port (
            A      : in std_logic_vector(3 downto 0);
                Y      : out std_logic_vector(1 downto 0);
            GS      : out std_logic
        );
    end component;

    signal a_tb      : std_logic_vector(3 downto 0);
    signal y_tb      : std_logic_vector(1 downto 0);
    signal gs_tb     : std_logic;

begin

    UUT : priority_encoder
        port map (
                                A      => a_tb,
                                Y      => y_tb,
                                GS     => gs_tb
        );

    stimulus: process
    begin

        a_tb    <= "0000";
        wait for 20 ns;

        a_tb    <= "0001";
        wait for 20 ns;

        a_tb    <= "0010";
        wait for 20 ns;

        a_tb    <= "0100";
        wait for 20 ns;

        a_tb    <= "1000";
        wait for 20 ns;
```

```
        wait ;  
    end process ;  
  
end behavioral ;
```

C Kotlin

C.1 roulette_software/src/main/kotlin/com/github/iselgt/roulette/UsbPort.kt

```
package com.github.iselgt.roulette
import isel.leic.UsbPort

fun main() {

    HAL.init()
    var counter = 0

    while (true) {

        val value = UsbPort.read()
        println("${counter++}: ${Integer.toBinaryString(value)}")

        Thread.sleep(500)
    }
}
```

C.2 roulette_software/src/main/kotlin/com/github/iselgt/roulette/HAL.kt

```
package com.github.iselgt.roulette

import isel.leic.UsbPort

object HAL {
    private var resetOutput = 0

    fun init(){
        resetOutput = 0
        UsbPort.write(resetOutput)
    }

    //Checks if the bit chosen by the mask is on
    fun isBit(mask: Int):Boolean {
        require(mask.countOneBits()==1){ "mask must be one bit only" }
        return UsbPort.read().and(mask) != 0
    }

    //Read the bits chosen by the mask and puts 0 on the bits that you aren't checking
    fun readBits(mask:Int):Int{
        return UsbPort.read().and(mask)
    }

    //Force 0 on the bits chosen by the mask
    fun clrBits(mask:Int) {
        resetOutput = resetOutput.and(mask.inv())
        UsbPort.write(resetOutput)
    }

    //Force 1 on the bits chosen by the mask
    fun setBits(mask:Int){
        resetOutput = mask.or(resetOutput)
        UsbPort.write(resetOutput)
    }

    //Chose the bits that u want to rewrite and force them with the input value
    fun writeBits(mask:Int, value:Int){
        clrBits(mask)
        setBits(value.and(mask))
    }
}
```

C.3 roulette_software/src/main/kotlin/com/github/iselgt/roulette/KBD.kt

```
package com.github.iselgt.roulette
import isel.leic.utils.Time

object KBD {

    const val EMPTY_CHAR = 0x00.toChar()    // and empty char
    private const val KVAL = 0x01           // Mask for Kval
    private const val K = 0x1E              // Mask for K
    private const val KACK = 0x01           // Mask for Kack

    private val keys =
        charArrayOf('1', '4', '7', '*', '2', '5', '8', '0',
                    '3', '6', '9', '#', 'A', 'B', 'C', 'D')

    fun init () {
        HAL.init()
    }

    private fun getKey(): Char {
        if (HAL.isBit(KVAL)) {
            val key = HAL.readBits(K)
            HAL.setBits(KACK)

            while(HAL.isBit(KVAL)) {}
            HAL.clrBits(KACK)
            return keys[key.shr(1)]
            // Need to use shr because of the K being in InputUsbPort(4-1)
        }
        return EMPTY_CHAR
    }

    fun waitKey(timeout : Long): Char {
        val endTime = timeout + Time.getTimeInMillis()
        var key: Char
        do {
            key = getKey()
        } while (Time.getTimeInMillis() < endTime && key == EMPTY_CHAR)
        return key
    }
}
```

C.4 roulette_software/src/main/kotlin/com/github/iselgt/roulette/LCD.kt

```
package com.github.iselgt.roulette

import isel.leic.utils.Time

object LCD {
    private const val LINES = 2
    private const val COLS = 16

    private const val SERIAL_INTERFACE = false

    // Useful Constants to use with LCD
    private const val NONE_VALUE = 0x00 // Null-Terminator value for when no k
    private const val DATA_MASK = 0x1E // A useful mask that correspond to th
    private const val ENABLE_MASK = 0x80 // A useful mask that correspond to en
    private const val REGISTER_SELECTOR_MASK = 0x40 // A useful mask that correspond to th

    private const val WAIT_FIRST_TIME = 15L
    private const val WAIT_TIME = 5L

    // LCD Command Constants
    private const val LCD_CLEAR = 0x01 // Clear display & reset cursor to (0,0)
    const val LCD_HOME = 0x02 // Return cursor to (0,0) without clearing display
    private const val LCD_ENTRY_MODE = 0x06 // Cursor moves right, no display shift
    private const val LCD_DISPLAY_OFF = 0x08 // Turn off display
    const val LCD_DISPLAY_ON = 0x0C // Display ON, Cursor OFF, Blink OFF
    const val LCD_DISPLAY_ON_CURSOR = 0x0E // Display ON, Cursor ON, No Blink
    private const val LCD_DISPLAY_ON_BLINK = 0x0F // Display ON, Cursor ON, Blink ON
    private const val LCD_FUNCTION_SET = 0x28 // 4-bit mode, 2 lines, 5x8 font

    // Cursor Positioning Constants
    private const val LCD_LINE_1 = 0x80 // First line
    private const val LCD_LINE_2 = 0xC0 // Second line

    // Mode Sets Bits Constants
    private const val SET4BITS = 0x2 // Entry Mode Set 4 bits long
    private const val SET8BITS = 0x3 // Entry Mode Set 8 bits long

    private fun writeDATA(data: Int) {
        writeByte(true, data)
    }

    private fun writeCMD(data: Int) {
        writeByte(false, data)
    }

    // Writes a Byte command/data on LCD
    private fun writeByte(rs: Boolean, data: Int) {
```

```
// The 4 most significant bits
val topdata = data shr 4
// The 4 less significant bits
val botdata = data and 0x0F

writeNibble(rs, topdata) // High
writeNibble(rs, botdata) // Low

}

// Writes a nibble command/data on LCD
private fun writeNibble(rs: Boolean, data: Int) {
    if (SERIAL_INTERFACE) writeNibbleSerial(rs, data.shl(1))
    else writeNibbleParallel(rs, data.shl(1))
}

// Writes a nibble (4 bits) of command/data to the LCD in Parallel Mode
private fun writeNibbleParallel(rs: Boolean, data: Int) {
    // Set or clear the Register Select (RS) pin depending on whether sending data or command
    if (rs) {
        HAL.setBits(REGISTER_SELECTOR_MASK) // RS = 1 for data
    }
    else {
        HAL.clrBits(REGISTER_SELECTOR_MASK) // RS = 0 for command
    }
    // Set the Enable (E) pin to high to latch the data
    HAL.setBits(ENABLE_MASK)

    // Send the 4-bit data by writing it to the data lines
    HAL.writeBits(DATA_MASK, data)

    // Hold Enable high for a short period to ensure the data is latched
    Time.sleep(WAIT_TIME)

    // Set the Enable (E) pin to low to complete the data transfer
    HAL.clrBits(ENABLE_MASK)

    // Wait again before the next operation
    Time.sleep(WAIT_TIME)
}

// Writes a nibble (4 bits) of command/data to the LCD in Serial Mode
private fun writeNibbleSerial(rs: Boolean, data: Int) {
    TODO()
}

fun init() {
```

```
// Initiate LCD with 8-bit mode before switching to 4-bit mode
Time.sleep(WAIT_FIRST_TIME) // Longer wait time for power-on
writeNibble(false, SET8BITS)
Time.sleep(WAIT_TIME)
writeNibble(false, SET8BITS)
Time.sleep(WAIT_TIME)
writeNibble(false, SET8BITS)

// Now switch to 4-bit mode
writeNibble(false, SET4BITS)

// Configure LCD settings using named constants
writeCMD(LCD_FUNCTION_SET) // 4-bit mode, 2-line, 5x8 font
writeCMD(LCD_DISPLAY_OFF) // Display OFF
writeCMD(LCD_CLEAR) // Clear display
Time.sleep(WAIT_TIME) // Extra delay needed for clearing
writeCMD(LCD_ENTRY_MODE) // Cursor moves right
writeCMD(LCD_DISPLAY_ON_BLINK) // Display ON, Cursor ON, Blink ON
Time.sleep(WAIT_TIME) // Short delay for stability
}

fun write(c: Char) {
    if (c != NONE_VALUE.toChar()) writeDATA(c.code)
}
//.code => .toInt()

fun write(text: String) {
    for (c in text) {
        write(c)
    }
}

fun cursor(line: Int, column: Int) {
    val address = when (line) {
        0 -> LCD_LINE_1 + column // First line
        1 -> LCD_LINE_2 + column // Second line
        else -> LCD_LINE_1 // Default to first line if invalid
    }
    writeCMD(address)
}

fun clear() {
    writeCMD(LCD_CLEAR)
    Time.sleep(WAIT_TIME)
}

fun main() {
    HAL.init()
}
```

```
LCD.init()  
while (true) {  
    LCD.write(KBD.waitKey(500))  
}  
}
```

C.5 roulette_software/src/main/kotlin/com/github/iselgt/roulette/TUI.kt

```
package com.github.iselgt.roulette

import isel.leic.utils.Time
import java.util.concurrent.TimeUnit

const val WAIT_TIME = 2L
const val WAIT_KEY = 200L

object TUI {
    fun init() {
        KBD.init()
        LCD.init()
    }

    fun writeMessage(msg: String){
        LCD.clear()
        LCD.write(msg)
    }
}

fun main() {

    TUI.init() // Initialize the TUI (Text User Interface) sy
    TUI.writeMessage("Hello World :)")
    Time.sleep(TimeUnit.SECONDS.toMillis(WAIT_TIME))// Pause the program for WAIT_TIME s
    LCD.clear()
    TUI.writeMessage("Grupo 11 Display")
    Time.sleep(TimeUnit.SECONDS.toMillis(WAIT_TIME))
    LCD.clear()
    TUI.writeMessage("Use '*' to Clear")

    var isCleared = false // Create a var that give us the information if the display wa

    while (true) {
        val key = KBD.waitKey(WAIT_KEY)
        if (key == '*') { // Chose the '*' char to be a shortcut for clearing the dis
            LCD.clear()
            isCleared = true
        }
        else { // Write the key after clearing and reset the flag
            if (isCleared) {
                LCD.write(key)
                isCleared = false // Reset the flag after writing the first key
            }
            else {
                LCD.write(key)
            }
        }
    }
}
```

}

}

D Kotlin_Tests

D.1 roulette_software/src/test/kotlin/HALTest.kt

```
package com.github.iselgt.roulette

import isel.leic.UsbPort
import kotlin.test.Test

class HALTest {

    @Test
    fun halGlobalTest() {

        HAL.init()
        var counter = 0x00

        while (true) {

            val value = UsbPort.read()
            HAL.setBits(7)
            println("${counter++}: ${Integer.toBinaryString(value)} | ${Integer.toBinaryString(
                Thread.sleep(500)
            )}
        }
    }
}
```

D.2 roulette_software/src/test/kotlin/KBDTest.kt

```
package com.github.iselgt.roulette

import com.github.iselgt.roulette.KBD.waitKey
import kotlin.test.Test

class KBDTest {

    @Test
    fun kbdTest() {
        KBD.init()

        while (true) {
            val keyPressed = waitKey(1000)
            if (keyPressed == KBD.EMPTY_CHAR) continue

            print(keyPressed)
        }
    }
}
```

D.3 roulette_software/src/test/kotlin/LCDTest.kt

```
package com.github.iselgt.roulette

import kotlin.test.Test

class LCDTest {

    @Test

    fun lcdTest(){
        LCD.init()
        while (true){
            val Key = KBD.waitKey(200)
            LCD.write(Key)
            if (Key == '*') {
                break
            }
        }
    }
}
```

E Pinos

	tatu	From	To	Assignment Name	Value	Enabled	Entity	Comment	Tag
1	✓		in Lin...[0]	Location	PIN_W5	Yes			
2	✓		in Lin...[1]	Location	PIN_AA14	Yes			
3	✓		in Lin...[2]	Location	PIN_W12	Yes			
4	✓		in Lin...[3]	Location	PIN_AB12	Yes			
5	✓		out Colss[0]	Location	PIN_AB11	Yes			
6	✓		out Colss[1]	Location	PIN_AB10	Yes			
7	✓		out Colss[2]	Location	PIN_AA9	Yes			
8	✓		out Colss[3]	Location	PIN_AA8	Yes			
9	✓		out Kout[0]	Location	PIN_A8	Yes			
10	✓		out Kout[1]	Location	PIN_A9	Yes			
11	✓		out Kout[2]	Location	PIN_A10	Yes			
12	✓		out Kout[3]	Location	PIN_B10	Yes			
13	✓		in Reset	Location	PIN_F15	Yes			
14	✓		in CLK	Location	PIN_P11	Yes			
15	✓		out LCD_RS	Location	PIN_W8	Yes			
16	✓		out LCD_EN	Location	PIN_V5	Yes			
17	✓		out LCD...[4]	Location	PIN_W11	Yes			
18	✓		out LCD...[5]	Location	PIN_AA10	Yes			
19	✓		out LCD...[6]	Location	PIN_Y8	Yes			
20	✓		out LCD...[7]	Location	PIN_Y7	Yes			

Figura 6: Atribuição dos pinos do roulette