

O módulo Serial Score Controller (SSC) implementa a interface com o mostrador de pontuação (Score Display), realizando a receção em série da informação enviada pelo módulo de controlo e entregando-a posteriormente ao mostrador de pontuação

1 Módulo SSC

 


Figura 1 – Diagrama de blocos do módulo Serial Score Controller e do Score Display

O módulo SSC recebe em série uma mensagem composta por sete (7) bits de informação e um (1) bit de paridade par, segundo o protocolo de comunicação. Os três primeiros bits de informação, indicam o comando a realizar no mostrador de pontuação. Os restantes quatro bits identificam o campo de dados. Tal como acontece com o SLCDC, o canal de receção série pode ser libertado após a receção da trama recebida pelo Score Display, não sendo necessário esperar pela sua execução do comando correspondente. Assim, o bloco Score Dispatcher pode ativar, prontamente, o sinal done para informar o bloco Serial Receiver que a trama já foi processada.

 


Figura 2 – Protocolo de comunicação do módulo Serial Score Controller

Cmd 2 1 0	data 3 2 1 0	Function
0 0 0	$d_3 d_2 d_1 d_0$	update digit 0
0 0 1	$d_3 d_2 d_1 d_0$	update digit 1
...
1 0 1	$d_3 d_2 d_1 d_0$	update digit 5
1 1 0	— — — —	update display
1 1 1	— — — 0	display on
1 1 1	— — — 1	display off

Figura 3 – Comandos do módulo Score Display

2 Score Display

O Score Display aceita três linhas de comando de entrada (cmd 2.. 0) e quatro linhas de dados de entrada (data 3.. 0). Os dados decodificados são conectados aos 7 pinos de saída que acionam os LEDs do display de 7 segmentos.

3 Interface com o Control

Implementou-se a classe ScoreDisplay em *software*, recorrendo a linguagem Kotlin, o bloco Serial Receiver e o bloco Score Dispatcher em *hardware*, recorrendo a linguagem VHDL.

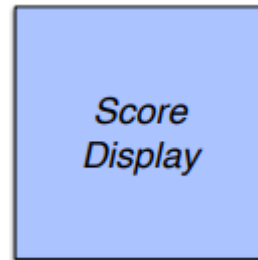


Figura 4- Classe Score Display

3.1 Classe Score Display

- Init, que inicia a classe
- SetScore, um comando para atualizar o valor value no mostrador da pontuação
- Off, envia um comando para ativar/desativar a visualização do mostrador de pontuação

4 Serial Receiver

O bloco Serial Receiver do módulo SLCDC é constituído por quatro blocos principais: i) um bloco de controlo; ii) um bloco conversor série paralelo; iii) um contador de bits recebidos; e iv) um bloco de validação de paridade, designados por Serial Control, Shift Register, Counter e Parity Check respetivamente.

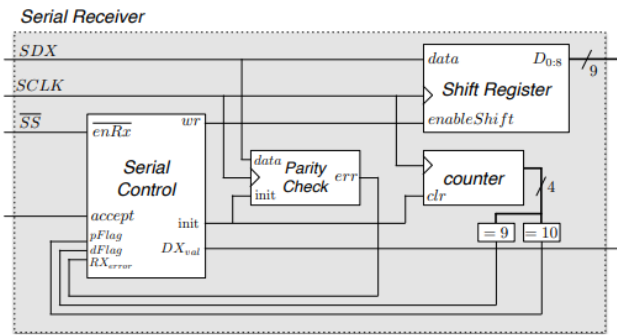


Figura 5 – Diagrama de blocos do bloco Serial Receiver

- O Serial Control é uma máquina de estados com 5 estados, Initializing, Starting, Waiting, Accepted e ItsDone. Começa por ativar o init no primeiro estado, dando assim init ao Parity Check (reset) e clear ao Counter, quando o sinal enRX tiver a '0', a máquina transita para o próximo estado Starting ativando o sinal wr, dando assim enableShift ao Shift Register.

Para transitar para o próximo estado Waiting, é feita novamente a verificação do sinal enRX, se este tiver o valor '1' retornará para o estado inicial Initializing, se o sinal enRX tiver a '0', e o sinal dFlag tiver a '1' será feita a transição.

Após isto, é feita novamente a verificação do sinal enRX, caso este esteja ativo, retornará para o estado inicial, Initializing se o sinal estiver a '0', é feita a verificação do sinal pFlag, se este tiver a '1', a máquina transita para o estado Accepted.

Neste estado, é feita uma verificação do sinal RXerror onde, caso este esteja ativo, retornará para o estado inicial Initializing, se o sinal estiver a '0', passará para o próximo e último estado ItsDone.

Neste último estado o sinal DXval é ativo e, é feita uma verificação do sinal Accept, caso este esteja a '1' retornará ao estado inicial.

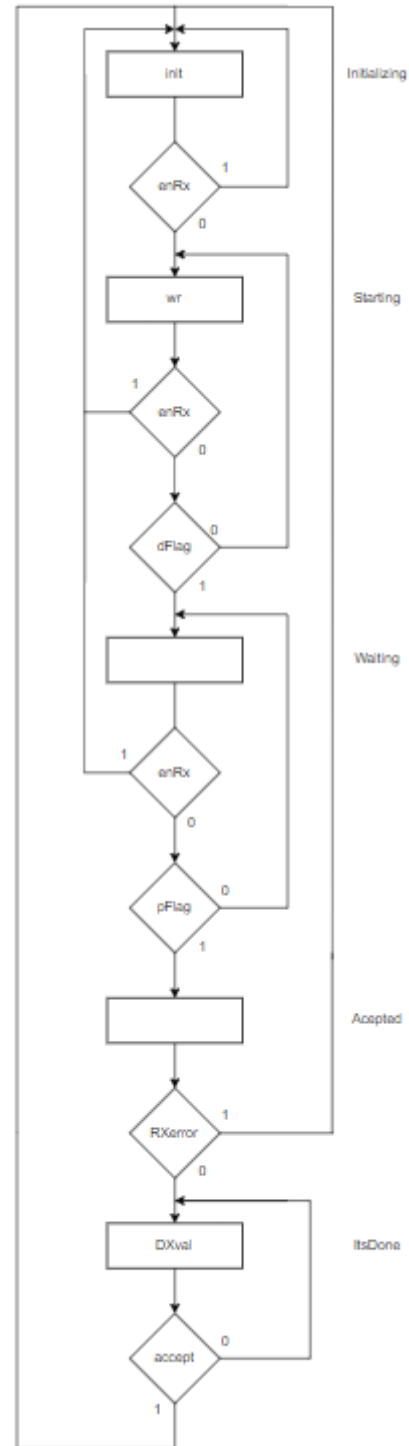


Figura 6 – Máquina de estados do Serial Control

5 Score Dispatcher

O bloco Score Dispatcher é responsável pela entrega das tramas válidas recebidas pelo bloco Serial Receiver ao Score Display, através da ativação do sinal *WrD*. Este bloco é apenas constituído pelo ScoreDisplayerControl.

O ScoreDisplayControl é uma máquina de estados com três estados, *WaitingDval*, *ReceivingDval* e *DoneReceived*. No primeiro estado *WaitingDval*, começa por verificar se o sinal *Dval* encontra-se a '1', se sim, significa que a trama foi recebida e a máquina transita para o próximo estado sendo este o *ReceivingDval*.

Neste estado, o sinal *WrD* é ativo e transita para o estado *DoneReceived* onde o sinal *WrD* deixa de estar ativo, deixando ativo o sinal *done* ativo, neste estado, o *Dval* é novamente verificado, porém neste caso se este tiver a '0' retornará para o estado inicial *WaitingDval*, significando que a trama já foi processada e a máquina poderá esperar por uma nova trama.

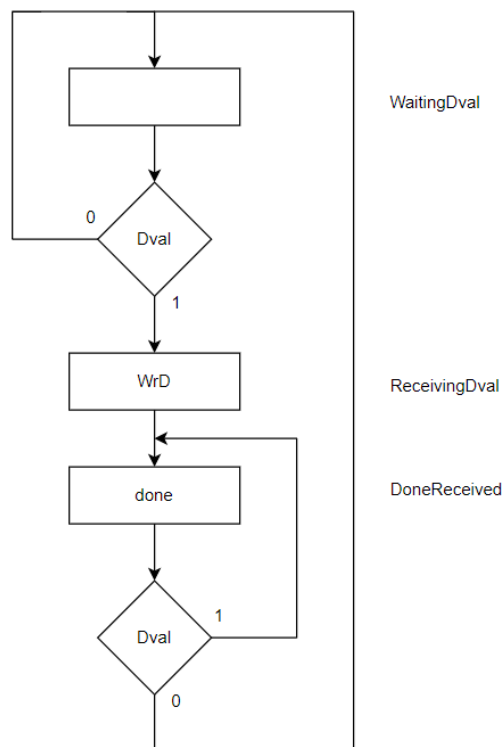


Figura 7- Máquina de estados Score Dispatcher Control

6 Conclusão

Com a implementação deste módulo foi possível a interação com o ScoreDisplay a partir de dois blocos: Serial Receiver e Score Dispatcher Control. Estes dois blocos têm a função de ler e transmitir a mensagem enviada pelo bloco de controlo até ao Score.

A. Descrição VHDL do bloco Serial Score Controller

Código VHDL do SSC:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity SSC is
port(
SS : in std_logic;
Reset : in std_logic;
SCLK : in std_logic;
Clk : in std_logic;
SDX : in std_logic;
WrD : out std_logic;
DoutSSC: out std_logic_vector(6 downto 0)
);
end SSC;

architecture structural of SSC is
component SerialReceiverSSC is
port(
Reset : in std_logic;
SDX : in std_logic;
Clk : in std_logic;
SCLK : in std_logic;
SS : in std_logic;
accept : in std_logic;
D : out std_logic_vector(6 downto 0);
DXval : out std_logic
);
end component;

component ScoreDispatcher is
port(
```

```
Dval : in std_logic;  
Din : in std_logic_vector(6 downto 0);  
WrD : out std_logic;  
Dout : out std_logic_vector(6 downto 0);  
done : out std_logic  
);  
end component;
```

```
signal DXVal_exit : std_logic;  
signal D_exit : std_logic_vector(6 downto 0);  
signal done_exit : std_logic;
```

```
begin
```

```
SD: ScoreDispatcher port map (Dval => DXVal_exit, Din => D_exit , done => done_exit, WrD => WrD, Dout =>  
DoutSSC);
```

```
SR : SerialReceiverSSC port map (Reset => Reset, SDX => SDX, Clk => Clk, SCLK => SCLK, SS => SS, accept =>  
done_exit, D => D_exit, DXval => DXval_exit);
```

```
end structural;
```

Código VHDL do ScoreDispatcher:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
entity ScoreDispatcher is  
    port(  
        Dval : in std_logic;  
        reset : in std_logic;  
        clk : in std_logic;  
        Din : in std_logic_vector(6 downto 0);  
        WrD : out std_logic;  
        Dout : out std_logic_vector(6 downto 0);  
        done : out std_logic  
    );  
end ScoreDispatcher;  
architecture structural of ScoreDispatcher is
```

```
component ScoreDispatcherControl is
    port(
        clk : in std_logic;
        reset : in std_logic;
        Dval : in std_logic;
        WrD : out std_logic;
        done : out std_logic
    );
end component;
begin
```

```
SD: ScoreDispatcherControl port map (Dval => Dval, done => done, WrD => WrD, reset => reset, clk => clk);
```

```
end structural;
```

Código VHDL do ScoreDispatcherControl:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity ScoreDispatcherControl is
    port(
        clk : in std_logic;
        reset : in std_logic;
        Dval : in std_logic;
        WrD : out std_logic;
        done : out std_logic
    );
end ScoreDispatcherControl;
architecture behavior of ScoreDispatcherControl is

    type STATE_TYPE is (WaitingDval, ReceivingDval, DoneReceived);

    signal currentState, nextState: STATE_TYPE;

begin
```

```
currentState <= WaitingDval when reset = '1' else NextState when rising_edge(clk);
```

```
GenerateNextState:
```

```
process(currentState, Dval)
```

```
begin
```

```
case currentState is
```

```
when WaitingDval => if (Dval = '1') then
```

```
NextState <= ReceivingDval;
```

```
else
```

```
NextState <= WaitingDval;
```

```
end if;
```

```
when ReceivingDval => NextState <= DoneReceived;
```

```
when DoneReceived => if (Dval = '1') then
```

```
NextState <= DoneReceived;
```

```
else
```

```
NextState <= WaitingDval;
```

```
end if;
```

```
end case;
```

```
end process;
```

```
WrD <= '1' when (CurrentState = ReceivingDval)
```

```
else '0';
```

```
done <= '1' when (CurrentState = DoneReceived)
```

```
else '0';
```

```
end behavior;
```

Código VHDL do SerialReceiverSSC:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
entity SerialReceiverSSC is
```

```
port(
```

```
Reset : in std_logic;
```

```
SDX : in std_logic;
```

```
Clk : in std_logic;
SCLK : in std_logic;
SS : in std_logic;
accept : in std_logic;
D : out std_logic_vector(6 downto 0);
DXval : out std_logic
);
end SerialReceiverSSC;
architecture structural of SerialReceiverSSC is
component ShiftRegisterSerialReceiverSSC is
port(
data: in std_logic;
SCLK: in std_logic;
E: in std_logic;
D: out std_logic_vector(6 downto 0)
);
end component;
component Counter is
port(
PL:in std_logic;
CE:in std_logic;
CLK:in std_logic;
Data_in: in std_logic_vector(3 downto 0);
RESET: in std_logic;
TC: out std_logic;
Q:out std_logic_vector(3 downto 0)
);
end component;
component ParityCheck is
port(
data : in std_logic;
Sclk : in std_logic;
init : in std_logic;
err : out std_logic
);
end component;
component SerialControl is
port(
```



```
enRx : in std_logic;
accept : in std_logic;
pFlag : in std_logic;
dFlag : in std_logic;
RXerror : in std_logic;
wr : out std_logic;
init : out std_logic;
Reset : in std_logic;
Clk : in std_logic;
DXval : out std_logic
);
end component;
component Equal7 IS
port(
Q: in STD_LOGIC_VECTOR(3 downto 0);
TC: out STD_LOGIC
);
end component;
component Equal6 IS
port(
Q: in STD_LOGIC_VECTOR(3 downto 0);
TC: out STD_LOGIC
);
end component;
```

```
signal ParitCheck_err_exit : std_logic;
signal SerialControl_init_exit : std_logic;
signal SerialControl_wr_exit : std_logic;
signal CounterSerialReceiver_exit : std_logic_vector(3 downto 0);
signal dflag_6: std_logic;
signal pflag_7: std_logic;
```

```
begin
```

```
Shift: ShiftRegisterSerialReceiverSSC port map (data=>SDX ,SCLK=>SCLK ,E => SerialControl_wr_exit ,D=>D);
```

Count: Counter port map (PL => '0', CE => '1', CLK => SCLK, Data_in => "0000", RESET => SerialControl_init_exit, Q => CounterSerialReceiver_exit);

Parity: ParityCheck port map (data => SDX, Sclk => SCLK, init => SerialControl_init_exit, err => ParitCheck_err_exit);

Controle: SerialControl port map (enRX => SS, accept => accept, pFlag => pflag_7, dFlag => dflag_6, RXerror => ParitCheck_err_exit, wr => SerialControl_wr_exit, init => SerialControl_init_exit, DXval => DXval, Clk => Clk, Reset => Reset);

EQ1: Equal6 port map(Q => CounterSerialReceiver_exit, TC => dflag_6);

EQ2: Equal7 port map(Q => CounterSerialReceiver_exit, TC => pflag_7);

end structural;

Código VHDL do ShiftRegisterSerialReceiverSSC:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity ShiftRegisterSerialReceiverSSC is
port(
data: in std_logic;
SCLK: in std_logic;
E: in std_logic;
D: out std_logic_vector(6 downto 0)
);
end ShiftRegisterSerialReceiverSSC;

architecture structural of ShiftRegisterSerialReceiverSSC is
component FFD IS
PORT(
CLK : in std_logic;
RESET : in STD_LOGIC;
SET : in std_logic;
D : IN STD_LOGIC;
EN : IN STD_LOGIC;
Q : out std_logic
);
end component;
```

```
signal saidaFFD1: std_logic;  
signal saidaFFD2: std_logic;  
signal saidaFFD3: std_logic;  
signal saidaFFD4: std_logic;  
signal saidaFFD5: std_logic;  
signal saidaFFD6: std_logic;  
signal saidaFFD7: std_logic;
```

```
begin
```

```
FFD1: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>data,   EN=>E,Q=>saidaFFD1);  
FFD2: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD1,EN=>E,Q=>saidaFFD2);  
FFD3: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD2,EN=>E,Q=>saidaFFD3);  
FFD4: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD3,EN=>E,Q=>saidaFFD4);  
FFD5: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD4,EN=>E,Q=>saidaFFD5);  
FFD6: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD5,EN=>E,Q=>saidaFFD6);  
FFD7: FFD port map(CLK=>SCLK,RESET=> '0' ,SET=> '0',D=>saidaFFD6,EN=>E,Q=>saidaFFD7);
```

```
D(6)<= saidaFFD1;  
D(5)<= saidaFFD2;  
D(4)<= saidaFFD3;  
D(3)<= saidaFFD4;  
D(2)<= saidaFFD5;  
D(1)<= saidaFFD6;  
D(0)<= saidaFFD7;
```

```
end structural;
```

Código VHDL do ScoreDisplay:

```
-----  
-----  
-- Project    : Score Display (Space Invaders Game)  
-- Affiliations: DEETC, ISEL - IPL  
-- Funding    : -  
-----  
-- File       : scoreDisplay.vhd  
-- Author(s)  : Pedro Miguens Matutino  
-- Date       : 2024/02/16  
-----
```

-- Copyright (c) 2024 Pedro Miguens Matutino

-- Description :

-- .

library ieee;

use ieee.std_logic_1164.all;

entity scoreDisplay is

port(
 set : in std_logic;
 cmd : in std_logic_vector(2 downto 0);
 data : in std_logic_vector(3 downto 0);
 HEX0 : out std_logic_vector(7 downto 0);
 HEX1 : out std_logic_vector(7 downto 0);
 HEX2 : out std_logic_vector(7 downto 0);
 HEX3 : out std_logic_vector(7 downto 0);
 HEX4 : out std_logic_vector(7 downto 0);
 HEX5 : out std_logic_vector(7 downto 0)
);

end scoreDisplay;

architecture structural of scoreDisplay is

component reg_4bit is

port(
 clk : in std_logic;
 reset : in std_logic;
 set : in std_logic;
 d : in std_logic_vector(3 downto 0);
 en : in std_logic;
 q : out std_logic_vector(3 downto 0)
);

end component;

component FFDScoreDisplay is

port(
 clk : in std_logic;
 reset : in std_logic;
 set : in std_logic;

```

        d : in std_logic;
        en : in std_logic;
        q : out std_logic
    );
end component;

component dec2hex is
port(    d : in std_logic_vector(3 downto 0);
        clear : in std_logic;
        dout: out std_logic_vector(7 downto 0)
    );
end component;

component dec_3_8 is
port( addr      :      in std_logic_vector(2 downto 0);
      en         :      in std_logic;
      dout       :      out std_logic_vector(7 downto 0)
    );
end component;

type register_array is array (0 to 5) of std_logic_vector(3 downto 0);
signal reg_values, out_values : register_array;
type seg_array is array (0 to 5) of std_logic_vector(7 downto 0);
signal display_values : seg_array;
signal en_digit : std_logic_vector(7 downto 0);
signal clear : std_logic;
begin

decoder : dec_3_8 port map(addr => cmd, en => '1', dout => en_digit);

circuit_gen : for ii in 0 to 5 generate
    in_reg      : reg_4bit      port map(clk => set, reset => '0' , set => '0', d => data, en => en_digit(ii), q =>
reg_values(ii));
    out_reg     : reg_4bit      port map(clk => set, reset => '0' , set => '0', d => reg_values(ii), en => en_digit(6),
q => out_values(ii));
    hex_digit   : dec2hex      port map(d => out_values(ii),clear => clear, dOut => display_values(ii));
end generate circuit_gen;

```

```
clear_reg: FFDScoreDisplay port map ( clk => set, reset => '0' , set => '0', en => en_digit(7), d => data(0), Q => clear);
```

```
HEX0 <= display_values(0);
```

```
HEX1 <= display_values(1);
```

```
HEX2 <= display_values(2);
```

```
HEX3 <= display_values(3);
```

```
HEX4 <= display_values(4);
```

```
HEX5 <= display_values(5);
```

```
end structural;
```

Código VHDL do ParityCheck:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
entity ParityCheck is
```

```
    port(
```

```
        data : in std_logic;
```

```
        Sclk : in std_logic;
```

```
        init : in std_logic;
```

```
        err : out std_logic
```

```
    );
```

```
end ParityCheck;
```

```
architecture structural of ParityCheck is
```

```
    component Counter is
```

```
        port(
```

```
            PL:in std_logic;
```

```
            CE:in std_logic;
```

```
            CLK:in std_logic;
```

```
            Data_in: in std_logic_vector(3 downto 0);
```

```
            RESET: in std_logic;
```

```
            TC: out std_logic;
```

```
            Q:out std_logic_vector(3 downto 0)
```

```
        );
```

```
end component;
```

```
signal SaidaB : std_logic_vector(3 downto 0);
```

begin

CounterUp : Counter port map (PL => '0', CE => data, CLK => Sclk, Data_in => "0000", Q => SaidaB, RESET => init);
err <= SaidaB(0);

end structural;

Código VHDL do SerialControl:

LIBRARY ieee;

USE ieee.std_logic_1164.all;

entity SerialControl is

port(

enRx : in std_logic;

RESET : in std_logic;

accept : in std_logic;

pFlag : in std_logic;

dFlag : in std_logic;

RXerror : in std_logic;

clk : in std_logic;

wr : out std_logic;

init: out std_logic;

DXval : out std_logic

);

end SerialControl;

architecture behavioral of SerialControl is

type STATE_TYPE is (Intializing, Starting, Waiting, Acepted, ItsDone);

signal currentState, NextState: STATE_TYPE;

begin

currentState <= Intializing when RESET = '1' else NextState when rising_edge(clk);

GenerateNextState:

process (currentState, enRx, accept, pFlag, RXerror, dFlag)

```

begin
    case currentState is
        when Initializing => if (enRx = '0') then
                                                    NextState    <=
Starting;
                                                    else
                                                    NextState    <=
Initializing;
                                                    end if;

        when Starting      => if (enRx = '1') then
                                                    NextState    <=
Initializing;
                                                    elsif (dFlag = '1') then
                                                    NextState    <=
Waiting ;
                                                    else
                                                    NextState    <=
Starting;
                                                    end if;

        when Waiting      => if (enRx = '1') then
                                                    NextState    <=
Initializing;
                                                    elsif (pFlag = '1') then
                                                    NextState    <=
Accepted;
                                                    else
                                                    NextState    <=
Waiting;
                                                    end if;

        when Accepted      => if (RXerror = '0') then
                                                    NextState    <=
ItsDone;
                                                    else
                                                    NextState    <=
Initializing;

```



```

end if;

when ItsDone => if(accept = '1') then
    NextState <=
        else
            NextState <=
        end if;
end case;
end process;

wr <= '1' when(currentState = Starting) else '0';
init <= '1' when(currentState = Initializing) else '0';
DXval <= '1' when (currentState = ItsDone) else '0';

end behavioral;

```

B. Código Kotlin – Score Display

```

object ScoreDisplay { // Controla o mostrador de pontuação.
    const val SS_SCORE = 0x02
    const val SCLK_SCORE = 0x10
    const val SDX_SCORE = 0x08

    // Inicia a classe, estabelecendo os valores iniciais.
    fun init() {
        SerialEmitter.init()
    }

    // Envia comando para atualizar o valor do mostrador de pontuação
    fun setScore(value: Int) { //ainda n esta validado
        val tamanho = value.toString().length
        var number = tamanho - 1
        var count = 0
        while (count < tamanho) {
            val bin = value.toString()[count].digitToInt()
            val valor = bin.shl(3) + number

```

```
        SerialEmitter.send(SerialEmitter.Destination.SCORE, valor, 7)
        number-=1
        count+=1
    }
    SerialEmitter.send(SerialEmitter.Destination.SCORE, 0b0000110, 7)
}
// Envia comando para desativar/ativar a visualização do mostrador de pontuação
fun off(value: Boolean) {
    if (value) {
        SerialEmitter.send(addr = SerialEmitter.Destination.SCORE, 0b0001111 ,
7)
        //tem haver com a tabela do projeto Tabela1 - Modulo Score Display
    } else {
        SerialEmitter.send(addr = SerialEmitter.Destination.SCORE, 0b0000111 ,
7)
    }
}
}
```