

O módulo *Keyboard Reader* é constituído por três blocos principais: i) o decodificador de teclado (*Key Decode*); ii) o bloco de armazenamento (designado por *Ring Buffer*); e iii) o bloco de entrega ao consumidor (designado por *Output Buffer*). Neste caso o módulo *Control*, implementado em *software*, é a entidade consumidora.


 



Figura 1 – Diagrama de blocos do módulo *Keyboard Reader*

1 Key Decode

O bloco *Key Decode* implementa um decodificador de um teclado matricial 4x3 por *hardware*, sendo constituído por três sub-blocos: i) um teclado matricial de 4x3; ii) o bloco *Key Scan*, responsável pelo varrimento do teclado; e iii) o bloco *Key Control*, que realiza o controlo do varrimento e o controlo de fluxo, conforme o diagrama de blocos representado na Figura 2a. O controlo de fluxo de saída do bloco *Key Decode* (para o módulo *Key Buffer*), define que o sinal *K_val* é ativado quando é detetada a pressão de uma tecla, sendo também disponibilizado o código dessa tecla no barramento *K_0:3*. Apenas é iniciado um novo ciclo de varrimento ao teclado quando o sinal *K_ack* for ativado e a tecla premida for libertada. O diagrama temporal do controlo de fluxo está representado na Figura 2b.

 

a) Diagrama de blocos

 

b) Diagrama temporal

Figura 2 – Bloco *Key Decode*

O bloco *Key Scan* foi implementado de acordo com o diagrama de blocos representado na Figura 3.

A implementação 1 foi selecionada por ser a mais fácil de colocar em prática, já que tem menos componentes individuais em comparação com as outras opções.

O módulo *Key Control* foi projetado com base em uma máquina de estados, conforme ilustrado na máquina de estados apresentada na Figura 4. Esta máquina opera em três estados principais: *Scanning*, *Pressing* e *Waiting*. O sinal *Kpress* é ativado quando uma tecla é pressionada, o sinal *Kack* é '1' quando a tecla pressionada é reconhecida e armazenada. O sinal *Kscan* é '1' durante o processo de varredura do teclado e, o sinal *Kpressa* a '0'. O sinal *Kval* indica que há um conjunto de dados pronto para ser transmitido e, o seu sinal passa a '1' quando encontra-se no estado *pressing*. A descrição *hardware* do bloco *Key Decode* em *VHDL* encontra-se no Anexo A.

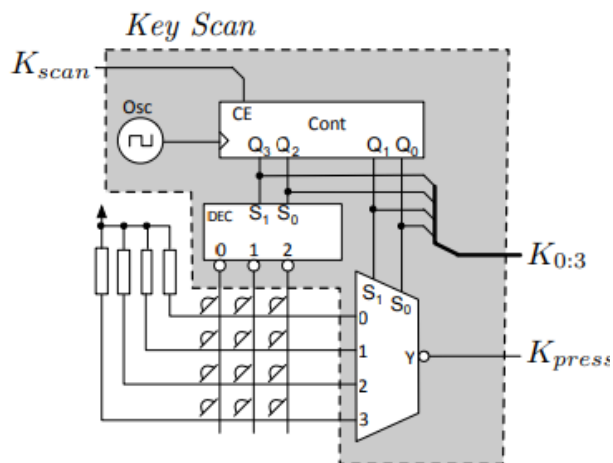


Figura 3 - Diagrama de blocos do bloco *Key Scan*

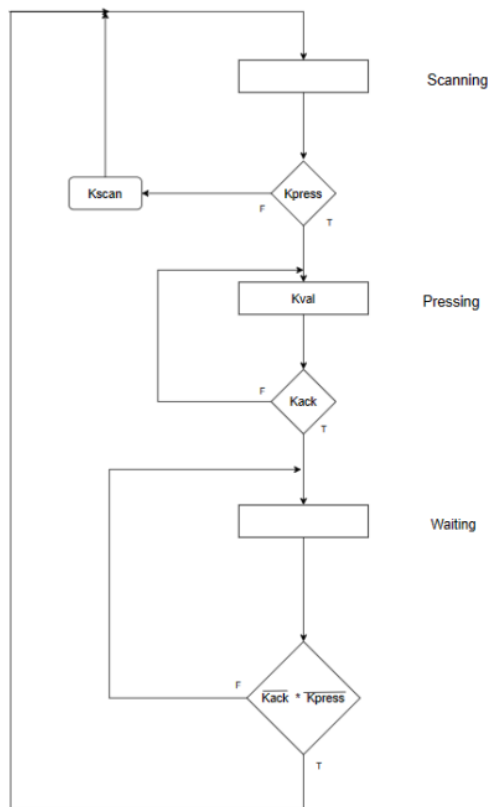


Figura 4 – Máquina de estados do bloco Key Control

Com base nas descrições do bloco Key Decode implementou-se parcialmente o módulo Keyboard Reader de acordo com o esquema eléctrico representado no anexo abaixo.

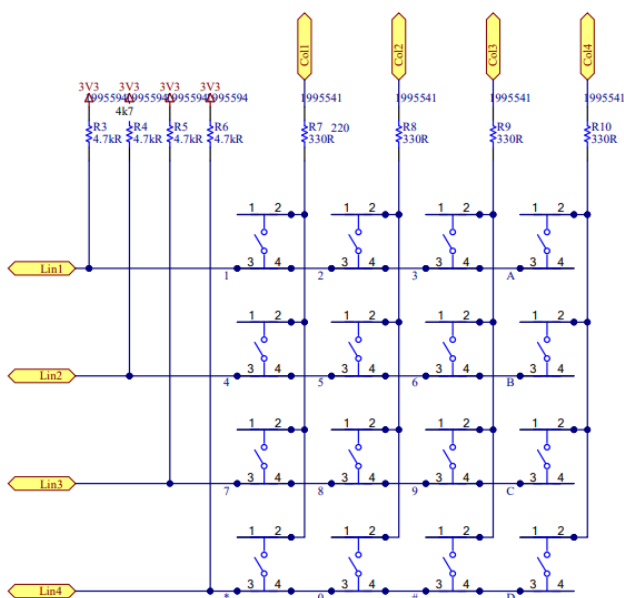


Figura 5 – Diagrama lógico do módulo Control de interface com o módulo Keyboard Reader

As classes HAL e KBD desenvolvidas são descritas nas secções 2.1. e 2.2, e o código fonte desenvolvido nos Anexos C e D, respetivamente.

2.1 Classe HAL

O HAL (Hardware Abstraction Layer) fornece uma interface simplificada para acessar o sistema UbsPort, permitindo que outros módulos de software interajam com o hardware de forma mais fácil e independentemente de detalhes específicos do dispositivo.

- `init`, que inicia a classe
- `isBit`, que recebe uma máscara como parâmetro do tipo inteiro e retorna `true` (boolean) se o bit analisado pela máscara tiver o valor '1'
- `readBits`, que recebe também uma máscara do tipo inteiro, que retorna os valores dos bits do UsbPort segundo a máscara
- `writeBits`, que recebe como parâmetros uma máscara e um valor, ambos inteiros, e que escreve no output os bits representados por mask e pelo valor
- `setBits`, que recebe uma máscara e coloca os bits representados pela mesma a '1' e escreve-os no output
- `clrBits`, que recebe também uma máscara e que faz o mesmo que a `setBits`, só que em vez de colocar os bits a '1', coloca '0'


2.2 Classe KBD

O KBD (Keyboard Reader) é encarregue de ler as teclas que são pressionadas e, em seguida, retornar o caractere correspondente à tecla pressionada. Os caracteres podem variar de '0' a '9', '#', '*' ou "NONE" se nenhuma tecla for pressionada.

- `init`, para iniciar a classe, que usa o `HAL.init`
- `getKey`, que retorna a tecla premida em formato char ou, caso nenhuma tecla esteja a ser premida, retorna NONE (valor 0, visto que NONE foi definido como um valor 0)
- `waitKey`, que recebe como parâmetro um timeout, do tipo Long, e retorna a tecla premida dentro do tempo do timeout

3 Ring Buffer

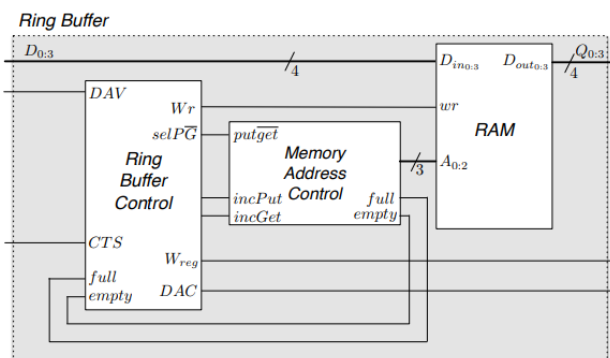O bloco Ring Buffer é uma estrutura de dados para armazenamento de teclas com disciplina FIFO (First In First Out), com capacidade de armazenar até oito palavras de quatro bits.



assim, a MAC vai fazer os seus ajustes no sinais full e empty, passando assim para o estado inicial isWaiting se o sinal DAV estiver inativo.

No estado IsWaiting, caso o DAV seja '0' ou o full seja '1', vai se verificar se o CTS(Clear to Send) está ativo e se o sinal empty está a '0', senão retornará para o próprio estado isWaiting, isto vai indicar que vamos fazer um "get" da RAM e vai ser lido uma palavra da memória sendo ativado o sinal Wreg e, se o sinal CTS já estiver inativo é ativado o sinal incGet, senão retornará ao próprio estado isWaiting.

- O MAC define o endereço de escrita/leitura, selecionado por *put \overline{get}* e é composto por 1 mux 2x1 e 3 counters, sendo o primeiro responsável pela contagem do sinal incPut, o segundo responsável pela contagem do sinal incGet e por fim, o terceiro sendo responsável pela incrementação ou decrementação.. Suporta assim ações de incPut e incGet, gerando informação se a estrutura de dados está cheia (Full) ou se está vazia (Empty).

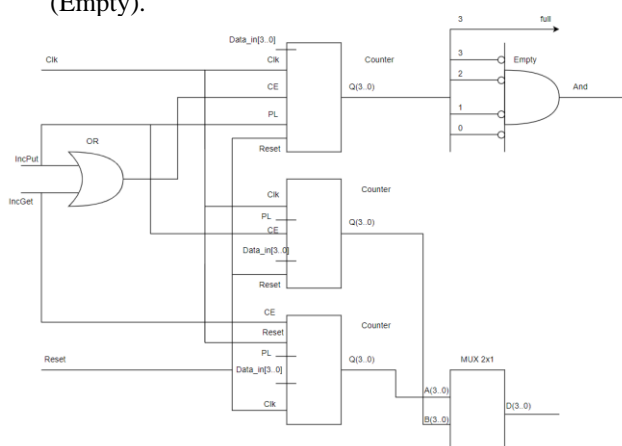


Figura 8- Diagrama de blocos do bloco MAC

com quatro bits (valor que é escrito na memória), *wr* e um *A* com três bits que vai indicar qual o endereço da memória a ler e tem como outputs um *Dout* com quatro bits.

4 Output Buffer

O bloco Output Buffer do Keyboard Reader é responsável pela interação com o sistema consumidor, neste caso o módulo Control, e indica se está disponível para armazenar dados através do sinal *OBfree*. Assim, nesta situação o sistema produtor pode ativar o sinal *Load* para registar os dados

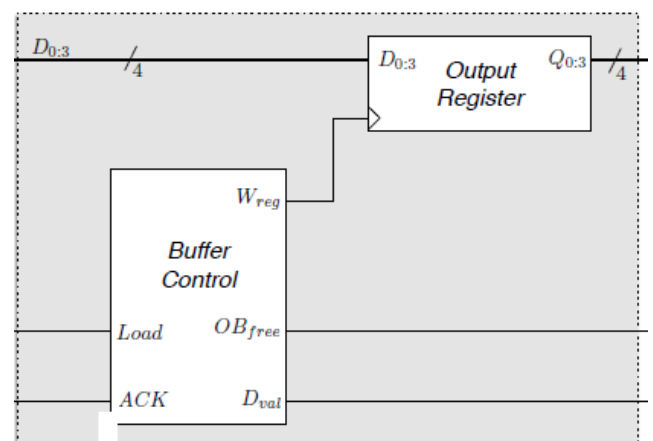


Figura 9- Diagrama de blocos do bloco Output Buffer

Contém dois blocos: o Buffer Control e o Output Register:

- A RAM é uma memória com capacidade para oito palavras de quatro bits e tem como inputs um *Din*

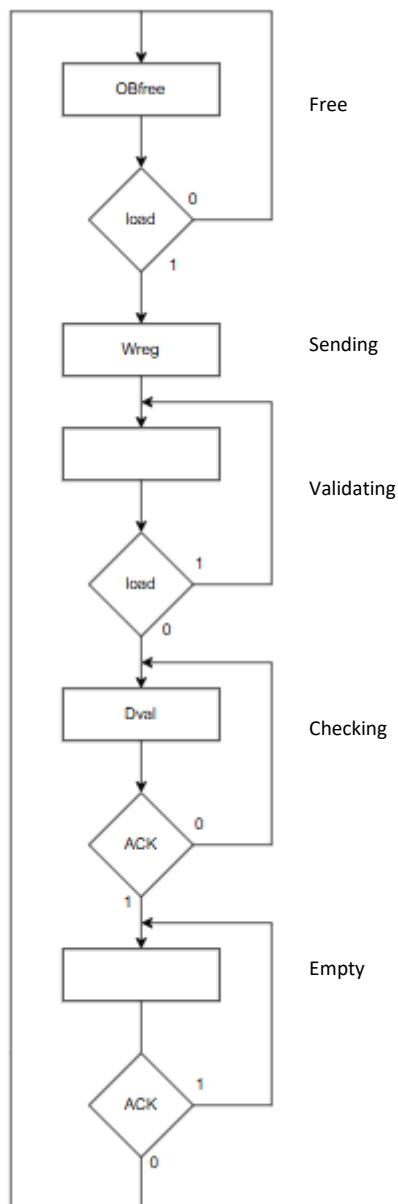


Figura 10– Máquina de estados do bloco *Buffer Control*

- O Buffer Control é uma máquina de estados com cinco estados, o Free, o Sending, o Validating, o Checking e o Empty. No primeiro estado, o sinal Obfree é ativo para armazenar dados, se o load estiver ativo, a máquina irá transitar de estado para Sending onde o Wreg será ativado para ativar o clock do Output Register, transitando assim para o próximo estado Validating, sendo este responsável por verificar se o sinal load ainda se encontra a '1', caso este esteja a '0', passa ao próximo estado, Cheking.

Neste estado o Dval será ativado para indicar que há um valor válido a ser recebido, verificando se o sinal ACK está a '1', sendo este ativo quando a informação chegar.

Por fim prossegue para o último estado Empty, sendo este responsável por verificar se a informação saiu, a partir do sinal ACK que caso esteja a '0' indica que a informação já partiu e retornando assim para o estado inicial

- O Output Register gerencia a transferência de dados do Output Buffer para o Control, garantindo que os dados sejam armazenados de forma segura até que possam ser utilizados.

5 Conclusão

Com este trabalho foi possível interligar a placa com o código em VHDL do Quartus, ao adicionarmos os blocos Ring Buffer e o OutPut Buffer ao Keyboard Reader já é possível armazenar várias teclas num Buffer e enviar para o bloco de controlo no momento certo. O teclado 4x3 da placa foi fácil de utilizar e tornou o trabalho bastante interativo.

A. Descrição VHDL do bloco *Key Decode*:

Código VHDL do KeyDecode:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity KeyDecode is
    port(
        Kack: in std_logic;
        Kval: out std_logic;
        KDecode : out std_logic_vector(3 downto 0);
        Lines : in std_logic_vector(3 downto 0);
        Cols : out std_logic_vector(2 downto 0);
        Clk : in std_logic;
        Reset : in std_logic
    );
end KeyDecode;

architecture structural of KeyDecode is
    component KeyScan is
        port(
            Kscan : in std_logic;
            Kpress : out std_logic;
            K : out std_logic_vector(3 downto 0);
            Lines : in std_logic_vector(3 downto 0);
            Cols : out std_logic_vector(2 downto 0);
            Osc : in std_logic;
            Reset : in std_logic
        );
    end component;

    component KeyControl is
        port(
            Kack : in std_logic;
            Kpress : in std_logic;
            clk: in std_logic;
            rst: in std_logic;
            Kval: out std_logic;
            Kscan: out std_logic
        );
    end component;
```

```
end component;

component ClkDiv is
    port(
        clk_in: in std_logic;
        clk_out: out std_logic
    );
end component;

signal SKscan : std_logic;
signal SKpress : std_logic;
signal Clock: std_logic;

begin
    Clocke : ClkDiv port map (clk_in => Clk, clk_out => Clock);
    Scan : KeyScan port map (Kscan => SKscan , K => KDecode, Kpress => SKpress , Lines => Lines, Cols => Cols ,
    Osc => Clock, Reset => Reset);
    Control : KeyControl port map (Kack => Kack, Kpress => SKpress, clk=>Clock ,rst => Reset ,Kval => Kval ,Kscan =>
    SKscan);

end structural;
```

Código VHDL do KeyScan:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity KeyScan is
    port(
        Kscan : in std_logic;
        Kpress : out std_logic;
        K : out std_logic_vector(3 downto 0);
        Lines : in std_logic_vector(3 downto 0);
        Cols : out std_logic_vector(2 downto 0);
        Osc : in std_logic;
        Reset : in std_logic
    );
end KeyScan;

architecture structural of KeyScan is
    component Counter is
```

```

        port
        (
            PL:in std_logic;
            CE:in std_logic;
            CLK:in std_logic;
            Data_in: in std_logic_vector(3 downto 0);
            RESET: in std_logic;
            TC: out std_logic;
            Q:out std_logic_vector(3 downto 0)
        );
end component;

component Decoder2x3 is
    port(
        Y : out std_logic_vector(2 downto 0);
        S0, S1 : in std_logic
    );
end component;

component mux4x1 is
    port(
        A : in std_logic_vector(3 downto 0);
        S0, S1 : in std_logic;
        Y : out std_logic
    );
end component;

signal interm_Q : std_logic_vector(3 downto 0);
signal Col : std_logic_vector(2 downto 0);
signal Yn : std_logic;

begin

Somador : Counter port map (Data_in(0) => '0', Data_in(1) => '0', Data_in(2) => '0',Data_in(3) => '0',PL=>'0',Clk =>
Osc , CE => Kscan, Reset => Reset, Q(0) => interm_Q(0) , Q(1) => interm_Q(1) , Q(2) => interm_Q(2) , Q(3) =>
interm_Q(3));

Decoder : Decoder2x3 port map (Y(0) => Col(0), Y(1) => Col(1), Y(2) => Col(2),S0 => interm_Q(2), S1 =>
interm_Q(3) );

Mux : mux4x1 port map (A=> Lines, S0 => interm_Q(0), S1 => interm_Q(1), Y => Yn);

K(0) <= interm_Q(0);
K(1) <= interm_Q(1);
K(2) <= interm_Q(2);

```



```
K(3) <= interm_Q(3);  
Cols <= not Col(2 downto 0);  
Kpress <= not Yn;
```

```
end structural;
```

Código VHDL do KeyControl:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
entity KeyControl is  
    port (  
        Kack : in std_logic;  
        Kpress : in std_logic;  
        clk: in std_logic;  
        rst: in std_logic;  
        Kval: out std_logic;  
        Kscan : out std_logic  
    );  
end KeyControl;  
architecture behavior of KeyControl is  
  
    type STATE_TYPE is (SCANNING, PRESSING, WAITING);  
  
    signal CurrentState, NextState: STATE_TYPE;  
  
begin  
  
    -- Flip-Flop's  
    CurrentState <= SCANNING when rst = '1' else NextState when rising_edge(clk);  
  
    -- Generate next state  
    Generatenextstate:  
    process (CurrentState, Kpress, Kack)  
        begin  
            case CurrentState is  
                when SCANNING => if (Kpress = '1') then
```

```

                                NextState <= PRESSING;
                                else
                                NextState <= SCANNING;
                                end if;

                                when PRESSING=> if (Kack = '0') then

                                NextState <= PRESSING;
                                else
                                NextState <= WAITING;
                                end if;

                                when WAITING => if (Kack = '0' and Kpress = '0') then

                                NextState <= SCANNING;
                                else
                                NextState <= WAITING;
                                end if;

                                end case;
                                end process;

                                -- Generate outputs
                                Kval <= '1' when (CurrentState = PRESSING)
                                else '0';

                                Kscan <= '1' when (CurrentState = SCANNING and Kpress = '0')
                                else '0';

                                end behavior;

```

Código VHDL do ClkDiv:

```

Library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;

entity ClkDiv is
generic(div: natural := 50000000);
port ( clk_in: in std_logic;

```

```
        clk_out: out std_logic);  
  
end ClkDiv;  
  
architecture bhv of ClkDiv is  
  
    signal count: integer:=1;  
    signal tmp : std_logic := '0';  
  
begin  
  
    process(clk_in)  
    begin  
  
        if(clk_in'event and clk_in='1') then  
            count <=count+1;  
            if (count = div/2) then  
                tmp <= NOT tmp;  
                count <= 1;  
            end if;  
        end if;  
    end process;  
  
    clk_out <= tmp;  
  
End bhv;
```

Código VHDL do Counter:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
entity Counter is  
    port  
    (  
        PL:in std_logic;  
        CE:in std_logic;  
        CLK:in std_logic;  
        Data_in: in std_logic_vector(3 downto 0);  
        RESET: in std_logic;
```

```
TC: out std_logic;
Q:out std_logic_vector(3 downto 0)
);
end counter;
architecture structural of counter is
component Mux2_1 is
    port(
        A: in std_logic_vector(3 downto 0);
        B: in std_logic_vector(3 downto 0);
        PL:in std_logic;
        D: out std_logic_vector(3 downto 0)
    );
end component;
component Registo_KeyScan is
    port(
        D:in std_logic_vector(3 downto 0);
        CE: in std_logic;
        CLK:in std_logic;
        RST:in std_logic;
        Q:out std_logic_vector(3 downto 0)
    );
end component;
component ADDER is
    port(
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);
        Ci : in std_logic;
        S : out std_logic_vector(3 downto 0);
        Co : out std_logic
    );
end component;

signal saidaMux: std_logic_vector(3 downto 0);
signal saidaReg: std_logic_vector(3 downto 0);
signal saidaSomador :std_logic_vector(3 downto 0);

begin
U1: Mux2_1 port map (A=>saidaSomador,B=>Data_in,PL=>PL,D=>saidaMux);
```

```
U2: Registo_KeyScan port map (CE=>CE, CLK=>CLK, D=>saidaMux, Q=>saidaReg,RST=>RESET);
U3: ADDER port map(A=>saidaReg, B(0)=>'1',B(1)=>'0',B(2)=>'0',B(3)=>'0',
S=>saidaSomador,Ci=>'0');
TC<=not Data_in(0) and not Data_in(1) and not Data_in(2) and not Data_in(3);
Q<=saidaReg;
end structural;
```

Código VHDL do Decoder2x3:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY Decoder2x3 IS
    port(
        Y : out std_logic_vector(2 downto 0);
        S0, S1 : in std_logic
    );
END Decoder2x3;

ARCHITECTURE arch_Decoder of Decoder2x3 is
begin
    Y(0) <= (not S0 and not S1);
    Y(1) <= (S0 and not S1);
    Y(2) <= (not S0 and S1);

end arch_Decoder;
```

Código VHDL do mux4x1:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mux4x1 IS
    port(
        A : in std_logic_vector(3 downto 0);
        S0, S1 : in std_logic;
        Y : out std_logic
    );
```

```
END mux4x1;
```

```
ARCHITECTURE arch_mux4x1 of mux4x1 is
```

```
begin
```

```
Y <= (not S0 and not S1 and A(0)) or (S0 and not S1 and A(1)) or (not S0 and S1 and A(2)) or (S0 and S1 and A(3));
```

```
end arch_mux4x1;
```

Código VHDL do Mux2_1:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
entity Mux2_1 is
```

```
port
```

```
(
```

```
A: in std_logic_vector(3 downto 0);
```

```
B: in std_logic_vector(3 downto 0);
```

```
PL: in std_logic;
```

```
D: out std_logic_vector(3 downto 0)
```

```
);
```

```
end Mux2_1;
```

```
architecture structural of Mux2_1 is
```

```
begin
```

```
D(0) <= (A(0) and not PL) or (B(0) and PL);
```

```
D(1) <= (A(1) and not PL) or (B(1) and PL);
```

```
D(2) <= (A(2) and not PL) or (B(2) and PL);
```

```
D(3) <= (A(3) and not PL) or (B(3) and PL);
```

```
end structural;
```

Código VHDL do FFD_KeyScan:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY FFD_KeyScan IS
```

```
PORT( CLK : in std_logic;
```

```
RESET : in STD_LOGIC;
```

```
        SET : in std_logic;  
        D : IN STD_LOGIC;  
        EN : IN STD_LOGIC;  
        Q : out std_logic  
    );  
end FFD_KeyScan;
```

architecture logicFunction OF FFD_KeyScan IS

begin

```
Q <= '0' when RESET = '1' else '1' when SET = '1' else D WHEN rising_edge(clk) and EN = '1';  
end logicFunction;
```

Código VHDL do Registo_KeyScan:

LIBRARY ieee;

Use ieee.std_logic_1164.all;

Entity Registo_KeyScan is

port(

```
    CLK : in std_logic;  
    CE : in std_logic;  
    RST : in std_logic;  
    D : in std_logic_vector(3 downto 0);  
    Q : out std_logic_vector(3 downto 0)  
);
```

end Registo_KeyScan;

ARCHITECTURE arch_Registo of Registo_KeyScan is

component FFD_KeyScan is

port(

```
    CLK : in std_logic;  
    RESET : in std_logic;  
    SET : in std_logic;  
    EN : in std_logic;  
    D : in std_logic;  
    Q : out std_logic  
);
```

end component;

begin

FF1 : FFD_KeyScan port map (SET => '0', CLK => CLK, EN => CE, D => D(0), Q => Q(0), RESET => RST);

FF2 : FFD_KeyScan port map (SET => '0', CLK => CLK, EN => CE, D => D(1), Q => Q(1), RESET => RST);

FF3 : FFD_KeyScan port map (SET => '0', CLK => CLK, EN => CE, D => D(2), Q => Q(2), RESET => RST);

FF4 : FFD_KeyScan port map (SET => '0', CLK => CLK, EN => CE, D => D(3), Q => Q(3), RESET => RST);

end arch_registo;

Código VHDL do ADDER:

LIBRARY ieee;

Use ieee.std_logic_1164.all;

Entity ADDER is

port(

A :in std_logic_vector(3 downto 0);

B :in std_logic_vector(3 downto 0);

S :out std_logic_vector(3 downto 0);

Ci :in std_logic;

Co :out std_logic

);

end ADDER;

architecture structural of ADDER is

component FADDER is

port(

A : in std_logic;

B : in std_logic;

Ci : in std_logic;

S : out std_logic;

CO : out std_logic

);

end component;


```
signal carry : std_logic_vector(3 downto 1);
```

```
begin
```

```
U1 : FADDER port map ( A => A(0), B => B(0), Ci => Ci, S => S(0), CO => carry(1));
```

```
U2 : FADDER port map ( A => A(1), B => B(1), Ci => carry(1), S => S(1), CO => carry(2));
```

```
u3 : FADDER port map ( A => A(2), B => B(2), Ci => carry(2), S => S(2), CO => carry(3));
```

```
u4 : FADDER port map ( A => A(3), B => B(3), Ci => carry(3), S => S(3), CO => CO);
```

```
end structural;
```

Código VHDL do HADDER:

```
LIBRARY ieee;
```

```
Use ieee.std_logic_1164.all;
```

```
Entity HADDER is
```

```
    port (
```

```
        A :in std_logic;
```

```
        B :in std_logic;
```

```
        R :out std_logic;
```

```
        Co :out std_logic
```

```
    );
```

```
end HADDER;
```

```
architecture STRUCTUHADDER of HADDER is
```

```
begin
```

```
Co <= B and A;
```

```
R <= A xor B;
```

```
end STRUCTUHADDER;
```

Código VHDL do FADDER:

```
LIBRARY ieee;
Use ieee.std_logic_1164.all;

Entity FADDER is
port
(
    A :in std_logic;
    B :in std_logic;
    Ci :in std_logic;
    S :out std_logic;
    CO :out std_logic
);
end FADDER;

architecture structural of FADDER is
component HADDER is
port
(
    A : in std_logic;
    B : in std_logic;
    R : out std_logic;
    Co: out std_logic
);
end component;

signal adder: std_logic;
signal carry: std_logic_vector(1 downto 0);

begin
U1: HADDER port map ( A => A, B => B, R => adder, Co => carry(0));
U2: HADDER port map ( A => adder, B => Ci, R => S, Co => carry(1));

Co <= carry(0) or carry (1);

end structural;
```

Código VHDL do KeyDecode_tb:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_arith.ALL;
USE ieee.std_logic_unsigned.all;

entity KeyDecode_tb is
end KeyDecode_tb;

    architecture behavior of KeyDecode_tb is
        component KeyDecode is
            port(
                Lines:in std_logic_vector(3 downto 0);
                Kack:in std_logic;
                Clk:in std_logic;
                Reset:in std_logic;
                Cols: out std_logic_vector(2 downto 0);
                KDecode: out std_logic_vector(3 downto 0);
                Kval: out std_logic
            );
        end component;

        signal Kack,Clk,Reset : std_logic := '0';
        signal Lines :std_logic_vector(3 downto 0) := "1111";
        signal Cols : std_logic_vector(2 downto 0) := "000" ;
        signal KDecode: std_logic_vector(3 downto 0) :="0000" ;
        signal Kval: std_logic := '0';

        begin

            Decode: KeyDecode port map (
                Lines=>Lines,
                Kack=>Kack,
                Clk=>Clk,
                Reset=>Reset,
                Cols=>Cols,
                KDecode=>KDecode,
                Kval=>Kval
            );

            Clk <= not Clk after 5 ns;

            tb:Process
            begin
```

```
wait for 10 ns;  
Reset<='1';  
Lines<="0111";  
wait for 10 ns;  
Reset<='0';  
wait for 30 ns;  
Kack<='1';  
wait for 10 ns;  
Kack<= '0';  
end process;  
end;
```

Código VHDL do KeyScan_tb:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.std_logic_arith.ALL;  
USE ieee.std_logic_unsigned.all;  
entity KeyScan_tb is  
end KeyScan_tb;  
architecture behavior of KeyScan_tb is  
component KeyScan is  
port(  
    Reset: in std_logic;  
    Osc: in std_logic;  
    Kscan: in std_logic;  
    Lines: in std_logic_vector(3 downto 0);  
    Cols: out std_logic_vector(2 downto 0);  
    K:out std_logic_vector(3 downto 0);  
    Kpress : out std_logic  
);  
end component;  
signal Reset,Osc, Kscan: std_logic := '0';  
signal Lines: std_logic_vector(3 downto 0) := "0000";  
signal Kpress: std_logic := '0';  
signal Cols: std_logic_vector(2 downto 0) := "000";  
signal K: std_logic_vector(3 downto 0) := "0000";  
begin
```

```
Scan: KeyScan port map(  
Reset => Reset,  
Osc=>Osc,  
Kscan => Kscan,  
Lines => Lines,  
Cols => Cols,  
K => K,  
Kpress => Kpress  
);  
Osc <= not Osc after 5 ns;  
tb:Process  
begin --110ns  
wait for 10 ns;  
Reset <= '1';  
Lines <= "1101";  
wait for 10 ns;  
Reset <= '0';  
Kscan <= '1';  
wait for 30 ns;  
Kscan <= '0';  
wait for 10 ns;  
Lines <= "1011";  
Kscan <= '1';  
wait for 50 ns;  
end process;  
end;
```

Código VHDL do KeyControl_tb:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.std_logic_arith.ALL;  
USE ieee.std_logic_unsigned.all;  
entity KeyControl_tb is  
end KeyControl_tb;  
architecture behavior of KeyControl_tb is  
component Key_control is  
port(  

```

```
Kack: in std_logic;
Kpress: in std_logic;
Kval: out std_logic;
Kscan: out std_logic;
clk: in std_logic;
rst: in std_logic
);
end component;
signal Kack,Kpress,clk,rst: std_logic := '0';
signal Kval: std_logic := '0';
signal Kscan: std_logic := '0';
begin
Control: Key_control port map(
    Kack=>Kack,
    Kpress=>Kpress,
    Kval=>Kval,
    Kscan=>Kscan,
    clk=>clk,
    rst=>rst
);
clk <= not clk after 5 ns;
tb:Process
begin
    wait for 10 ns;
    rst<='1';
    wait for 10 ns;
    rst<='0';
    wait for 10 ns;
    Kpress<= '1';
    wait for 10ns;
    Kack<= '1';
    wait for 10ns;
    Kack<= '0';
    Kpress<= '1';
    wait for 10ns;
    Kpress<= '0';
end process;
end;
```

Código VHDL do ADDER_tb:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_arith.ALL;
USE ieee.std_logic_unsigned.all;

entity ADDER_tb is
end ADDER_tb;

architecture behavior of ADDER_tb is
component ADDER is
    port(
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);
        Ci : in std_logic;
        S : out std_logic_vector(3 downto 0);
        Co : out std_logic
    );
end component;

signal A,B: std_logic_vector(3 downto 0) := "0000";
signal Ci: std_logic := '0';
signal Co: std_logic := '0';
signal S: std_logic_vector(3 downto 0) := "0000";

begin
    ADD: ADDER port map(
        A=>A,
        B=>B,
        Ci=>Ci,
        S=>S,
        Co=>Co
    );

    tb:Process
    begin
        wait for 10 ns;
        A<="0010";
        B<="0101";
        Ci <= '0';
        wait for 10 ns;
        A<="1000";
```

```
B<= "0101";  
Ci <= '1';  
wait for 10 ns;  
A<="1100";  
B<= "0101";  
Ci <= '0';  
end process;  
end;
```

Código VHDL do Counter_tb:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
entity Counter_tb is  
end Counter_tb;  
  
architecture behavior of Counter_tb is  
  
    component Counter is  
        port  
        (  
            PL:in std_logic;  
            CE:in std_logic;  
            CLK:in std_logic;  
            Data_in: in std_logic_vector(3 downto 0);  
            RESET: in std_logic;  
            TC: out std_logic;  
            Q:out std_logic_vector(3 downto 0)  
        );  
    end component;  
  
    signal PL, CE, CLK, RESET: std_logic := '0';  
    signal Data_in: std_logic_vector(3 downto 0) := "0000";  
    signal TC: std_logic;  
    signal Q: std_logic_vector(3 downto 0);  
  
begin
```


UUT: Counter port map(

PL => PL,

CE => CE,

CLK => CLK,

Data_in => Data_in,

RESET => RESET,

TC => TC,

Q => Q

);

CLK <= not CLK after 5 ns;

tb: process

begin

wait for 10 ns;

RESET <= '1';

wait for 10 ns;

RESET <= '0';

wait for 10 ns;

PL <= '1';

wait for 10 ns;

CE <= '1';

wait for 10 ns;

Data_in <= "0001";

wait for 10 ns;

CE <= '0';

wait for 10 ns;

PL <= '0';

wait for 10 ns;

Data_in <= "0010";

wait for 10 ns;

Data_in <= "0100";

wait for 10 ns;

Data_in <= "1000";

wait for 10 ns;

CE <= '1';

wait for 10 ns;

```
CE <= '0';  
wait for 10 ns;  
RESET <= '1';  
wait for 10 ns;  
RESET <= '0';  
end process;
```

```
end behavior;
```

Código VHDL do Decoder2x3_tb:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```

```
ENTITY Decoder2x3_tb IS  
END Decoder2x3_tb;
```

```
ARCHITECTURE behavior OF Decoder2x3_tb IS
```

```
    COMPONENT Decoder2x3 IS  
    PORT(  
        Y : out std_logic_vector(2 downto 0);  
        S0, S1 : in std_logic  
    );  
END COMPONENT;
```

```
    SIGNAL S0, S1 : std_logic := '0';  
    SIGNAL Y : std_logic_vector(2 downto 0);
```

```
BEGIN
```

```
    UUT: Decoder2x3 PORT MAP(  
        Y => Y,  
        S0 => S0,  
        S1 => S1  
    );
```

```
tb: PROCESS
```

BEGIN

wait for 10 ns;

S0 <= '0';

S1 <= '0';

wait for 10 ns;

S0 <= '1';

S1 <= '0';

wait for 10 ns;

S0 <= '0';

S1 <= '1';

wait for 10 ns;

S0 <= '1';

S1 <= '1';

wait for 10 ns;

S0 <= '0';

S1 <= '0';

wait for 10 ns;

S0 <= '1';

S1 <= '0';

wait for 10 ns;

S0 <= '0';

S1 <= '1';

wait for 10 ns;

S0 <= '1';

S1 <= '1';

END PROCESS;

END behavior;

Código VHDL do mux4x1_tb:

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY mux4x1_tb IS

END mux4x1_tb;

ARCHITECTURE behavior OF mux4x1_tb IS

```
COMPONENT mux4x1 IS
```

```
  PORT(
```

```
    A : in std_logic_vector(3 downto 0);
```

```
    S0, S1 : in std_logic;
```

```
    Y : out std_logic
```

```
  );
```

```
END COMPONENT;
```

```
SIGNAL A : std_logic_vector(3 downto 0) := "0000";
```

```
SIGNAL S0, S1 : std_logic := '0';
```

```
SIGNAL Y : std_logic;
```

```
BEGIN
```

```
  UUT: mux4x1 PORT MAP(
```

```
    A => A,
```

```
    S0 => S0,
```

```
    S1 => S1,
```

```
    Y => Y
```

```
  );
```

```
tb: PROCESS
```

```
  BEGIN
```

```
    wait for 10 ns;
```

```
    S0 <= '0';
```

```
    S1 <= '0';
```

```
    wait for 10 ns;
```

```
    S0 <= '1';
```

```
    S1 <= '0';
```

```
    wait for 10 ns;
```

```
    S0 <= '0';
```

```
    S1 <= '1';
```

```
    wait for 10 ns;
```

```
    S0 <= '1';
```

```
    S1 <= '1';
```

```
    wait for 10 ns;
```

```
    A <= "0001";
```

```
wait for 10 ns;  
A <= "0010";  
wait for 10 ns;  
A <= "0100";  
wait for 10 ns;  
A <= "1000";  
wait for 10 ns;  
S0 <= '0';  
S1 <= '0';  
wait for 10 ns;  
S0 <= '1';  
S1 <= '0';  
wait for 10 ns;  
S0 <= '0';  
S1 <= '1';  
wait for 10 ns;  
S0 <= '1';  
S1 <= '1';  
END PROCESS;
```

```
END behavior;
```

B. Atribuição de pinos do módulo *Keyboard Reader*

```
set_global_assignment -name FAMILY "MAX 10 FPGA"  
set_global_assignment -name DEVICE 10M50DAF484C6GES  
set_global_assignment -name TOP_LEVEL_ENTITY "DE10_Lite"
```

#linhas

```
set_location_assignment PIN_W5 -to Lines[0]  
set_location_assignment PIN_AA14 -to Lines[1]  
set_location_assignment PIN_W12 -to Lines[2]  
set_location_assignment PIN_AB12 -to Lines[3]
```

#colunas

```
set_location_assignment PIN_AB11 -to Cols[0]  
set_location_assignment PIN_AB10 -to Cols[1]  
set_location_assignment PIN_AA9 -to Cols[2]
```

#Leds

```
set_location_assignment PIN_A8 -to QValue[0]  
set_location_assignment PIN_A9 -to QValue[1]  
set_location_assignment PIN_A10 -to QValue[2]  
set_location_assignment PIN_B10 -to QValue[3]  
set_location_assignment PIN_D13 -to Dval
```

#sw

```
set_location_assignment PIN_C11 -to Reset  
set_location_assignment PIN_D12 -to ACK
```

C. Código Kotlin - HAL

```
import isel.leic.UsbPort
// Virtualiza o acesso ao sistema UsbPort
object HAL {
    var lastOutput = 0
    // Inicia a classe
    fun init () {
        lastOutput = 0
        UsbPort.write(lastOutput)
    }
    // Retorna true se o bit tiver o valor lógico '1'
    fun isBit (mask:Int) : Boolean {
        return UsbPort.read().and(mask) != 0
    }
    // Retorna os valores dos bits representados por mask presentes no UsbPort
    fun readBits(mask: Int): Int{
        return UsbPort.read().and(mask)
    }
    // Escreve nos bits representados por mask os valores dos bits correspondentes
    em value
    fun writeBits(mask: Int, value: Int) {
        clrBits(mask)
        setBits(value and mask)
    }
    // Coloca os bits representados por mask no valor lógico '1'
    fun setBits (mask: Int) {
        lastOutput = mask.or(lastOutput)
        UsbPort.write(lastOutput)
    }
    // Coloca os bits representados por mask no valor lógico '0'
    fun clrBits(mask:Int) {
        lastOutput = lastOutput.and(0xFF - mask)
        UsbPort.write(lastOutput)
    }
}
```

D. Código Kotlin - KBD

```
import isel.leic.utils.Time
// Ler teclas. Métodos retornam '0'..'9', '#', '*' ou NONE.
object KBD {
    const val KEY = 0X0F
    const val NONE = ' '
    const val KACK_MASK = 0X80
    const val KVAL_MASK = 0X10
    val keys: CharArray = charArrayOf('1', '4', '7', '*', '2', '5', '8', '0', '3',
    '6', '9', '#')

    fun init() { //Inicia a classe
        HAL.init()
    }
    //Retorna de imediato a tecla premida ou NONE se não há tecla premida.
    fun getKey(): Char {
        if (HAL.isBit(KVAL_MASK)) {
            val tecla = HAL.readBits(KEY)
            HAL.setBits(KACK_MASK)
            if (!HAL.isBit(KVAL_MASK)) {
                HAL.clrBits(KACK_MASK)
                return keys[tecla]
            }
        }
        return NONE
    }
    //Retorna a tecla premida, caso ocorra antes do 'timeout' (representado em
    //milissegundos), ou NONE caso contrário.
    fun waitKey(timeout: Long): Char {
        val timeFinal = timeout + Time.getTimeInMillis() //tempo atual em
        //milissegundos + timeout
        var key = NONE
        do {
            key = getKey()
        } while (Time.getTimeInMillis() < timeFinal && key == NONE)
        return key
    }
}
```